



# Computer Hardware Engineering (IS1200)

## Computer Organization and Components (IS1500)

Fall 2020


### Lecture 7: Combinational Logic

*Note: This lecture is optional for IS1200 (for review only)*

Artur Podobas

Researcher, KTH Royal Institute of Technology

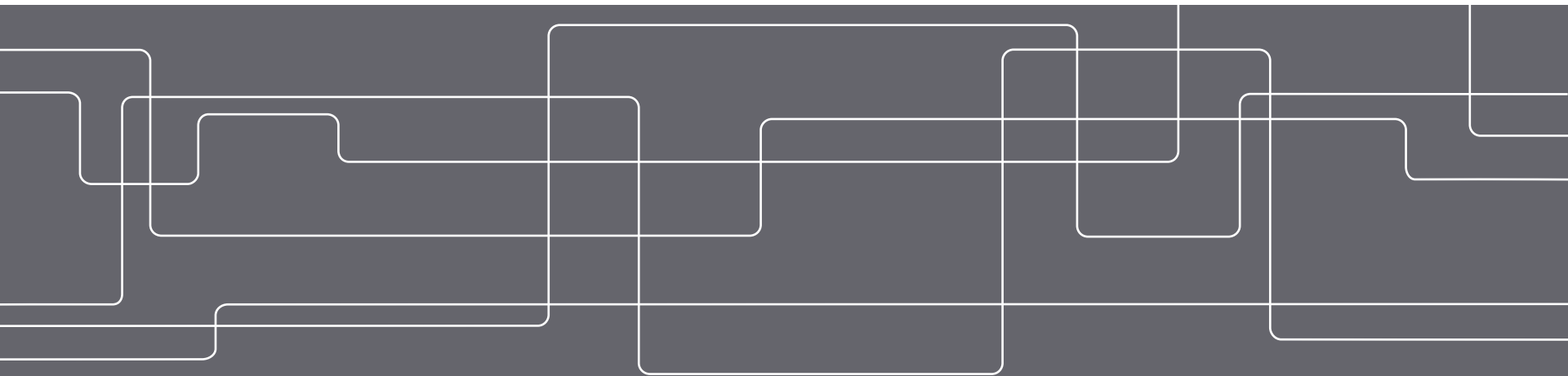Slides by David Broman (extensions by Artur Podobas), KTH






# Course Structure



## Module 1: C and Assembly Programming

 


## Module 2: I/O Systems



## Module 3: Logic Design (IS1500 only)


**PROJ  
START**

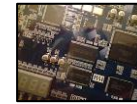

## Module 4: Processor Design



## Module 5: Memory Hierarchy

 

## Module 6: Parallel Processors and Programs



**Proj. Expo**


LE14

**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo

# Abstractions in Computer Systems

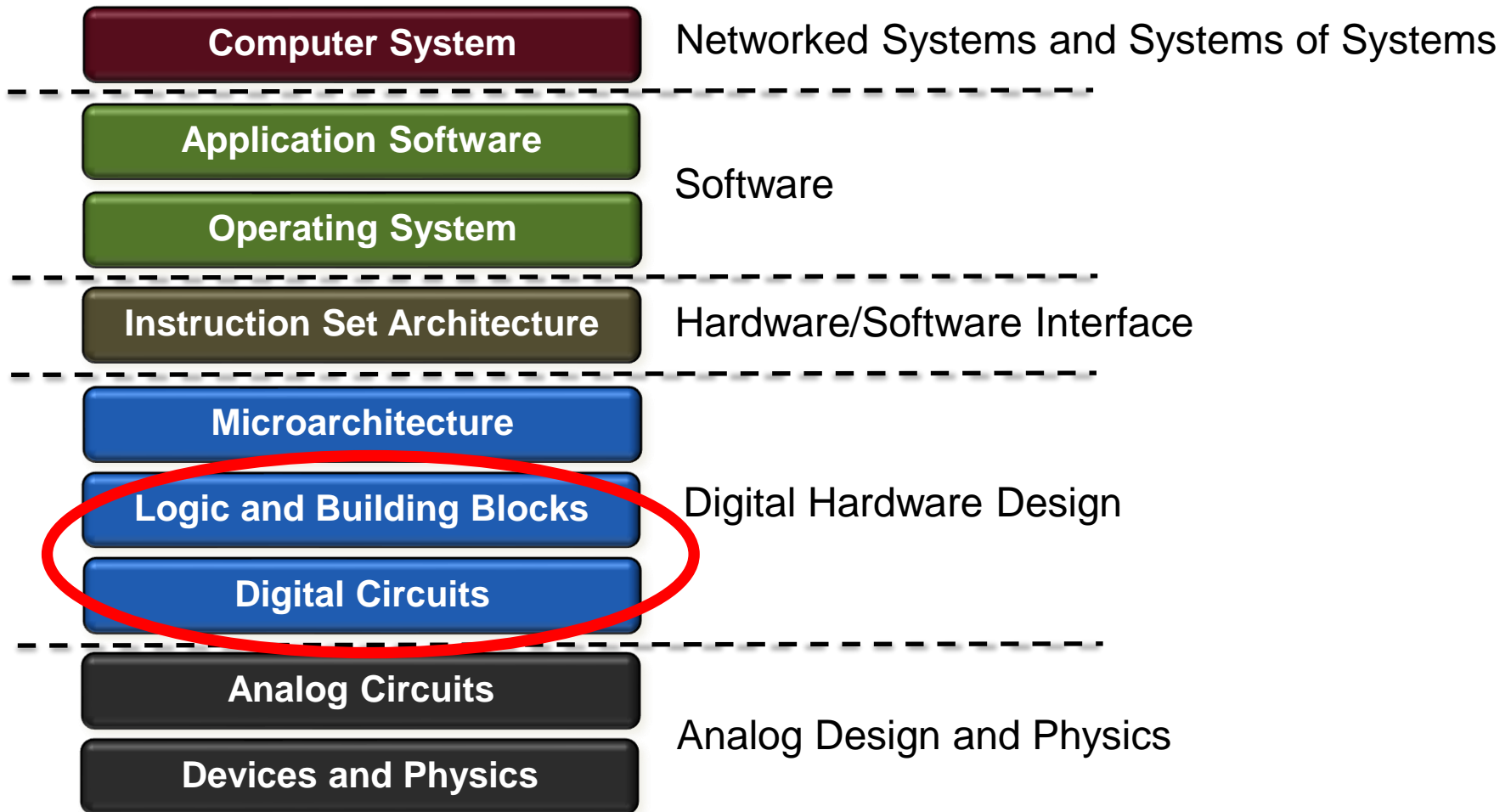

**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo



# Agenda

## Part I

### Gates and Boolean Algebra




## Part II

### Building Blocks: Multiplexers, Decoders, and Adders



## Part III

### Logisim Demo

 

**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo

# Part I

## Gates and Boolean Algebra



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.



**Part I**  
Gates and  
Boolean Algebra


**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo

# Logic Gates (1/3)


## AND, OR, NOT, and BUF

**AND**

 


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

**OR**

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**NOT**

 


The small circle (called a *bubble*) inverses the signal.

A	Y
0	1
1	0

**NOT** is also called an *inverter*.

**BUF**

 

Looks like **not**, but has no circle.

A	Y
0	0
1	1

**Buffer.** Logically the same as a wire. Relevant from an analog point of view.



**Part I**

Gates and  
Boolean Algebra

**Part II**

Building Blocks: Multiplexers,  
Decoders, and Adders


**Part III**

Logisim  
Demo

# Logic Gates (2/3)

## NAND, NOR, XOR, and XNOR


**NAND**

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

**NOT AND.** Note the  
Small bubble at the end.


**NOR**

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

**NOT OR.**

**XOR**

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

**Exclusive OR,**  
pronounced "ex-or".



**XNOR**



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

**Exclusive NOT OR.**



**Part I**  
Gates and  
Boolean Algebra


**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo


# Logic Gates (3/3)
 
## Multi-Input Logic Gates


Gates can be generalized to have more than two inputs. For instance:



**AND** gate with 3 inputs.

 

**NOT OR** gate with 5 inputs.

 

**Exclusive OR** gate with 3 inputs.



An N-input XOR gate is also called a **parity gate**. It outputs 1 when odd number of inputs are 1.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1





# Combinational Circuit

  

This circuit is **combinational** because its outputs depend *only* on its inputs. The circuit is *memoryless*, that is, it has no memory.



We will introduce memories in Lecture 8

Observe that this (rather useless) circuit always outputs 1. As a logic formula, this is called a **tautology**.




**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo

# Combinational Circuit

 


What is the result  
of Y and Z?



# Problematic Circuits


## Unstable circuit.

 

What is the value of Q?

**Answer:** it oscillates. This circuit is called a **ring oscillator**.

## Illegal value (X)

 

What is the value of Q?


**Answer:**  $Q = X$ , called an unknown or illegal value. For example, when a wire is driven to both 0 and 1 at the same time.

This situation is called **contention**.


 
# Floating Values and Tristate Buffers

A **tristate (or three-state) buffer** has high impedance if the **output enable** signal  $E$  is not active.



$E$	$A$	$Y$
0	0	Z
0	1	Z
1	0	0
1	1	1

Commonly used in **buses** when connecting multiple chips. If the buffers are not enabled at the same time, contention is avoided.

When the enable signal is not active, the output is said to be **floating** (using symbol Z).



# Boolean Algebra (1/4)

## Truth Tables and Sum-of-Products Form

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

A **truth table** with random output (we have seen them before).

We can create a boolean expression from the truth table

$$\bar{A}B\bar{C} + A\bar{B}C + AB\bar{C}$$

The line over a variable is called the **complement** and is the inverse of the variable (NOT). Sometimes a prime ' is used instead.

The **AND** of one or more variables is called a **product**.

**AND** can be written using "no space" or using a dot, e.g.  $A \cdot B \cdot C$

**OR** is written using the + symbol.

This form is called **sum-of-products** (surprise!)



**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo



# Boolean Algebra (1/4)

## Truth Tables and Sum-of-Products Form

$b_2 b_1 b_0$	$y_1 z_0$
0000	1 1
0001	1 0
0010	0 1
0011	0 1
1100	0 0
1101	0 0
1110	0 0
1111	0 0

**Count leading zeroes:** Given a bit vector  $b_2 b_1 b_0$ , count the number of leading zeroes and output as  $c_1 c_0$ .

$$Y = \overline{ABC} + \overline{A}BC$$

$$Z = \overline{ABC} + \overline{A}B\overline{C} + \overline{A}BC$$



# Boolean Algebra (2/4)

## Some Theorems

Theorem	Dual	Name
$A \cdot 1 = A$	$A + 0 = A$	Identity
$A \cdot 0 = 0$	$A + 1 = 1$	Null Element
$A \cdot A = A$	$A + A = A$	Idempotency
$\overline{\overline{A}} = A$		Involution
$A \cdot \overline{A} = 0$	$A + \overline{A} = 1$	Complements
$A \cdot B = B \cdot A$	$A + B = B + A$	Commutativity
$(A \cdot B) \cdot C = A \cdot (B \cdot C)$	$(A + B) + C = A + (B + C)$	Associativity
$(A \cdot B) + (A \cdot C) = A \cdot (B + C)$	$(A + B) \cdot (A + C) = A + (B \cdot C)$	Distributivity

Note! Not as traditional algebra

### Exercise:

Derive the simplest form of expression

$$BA + A\overline{B} + A$$

### Solution:

$$BA + A\overline{B} + A$$

$$= AB + A\overline{B} + A \quad \text{Commutativity}$$

$$= A(B + \overline{B}) + A \quad \text{Distributivity}$$

$$= A \cdot 1 + A \quad \text{Complements (dual)}$$

$$= A + A \quad \text{Identity}$$

$$= A \quad \text{Idempotency (dual)}$$



# Boolean Algebra (3/4)


## De Morgan's Theorem

### Theorem

$$\overline{A_1 \cdot A_2 \cdot A_3 \dots} = (\overline{A_1} + \overline{A_2} + \overline{A_3} \dots)$$


 
### Dual

$$\overline{A_1 + A_2 + A_3 \dots} = (\overline{A_1} \cdot \overline{A_2} \cdot \overline{A_3} \dots)$$



Augustus De Morgan  
British mathematician and  
logician (1806 – 1871).

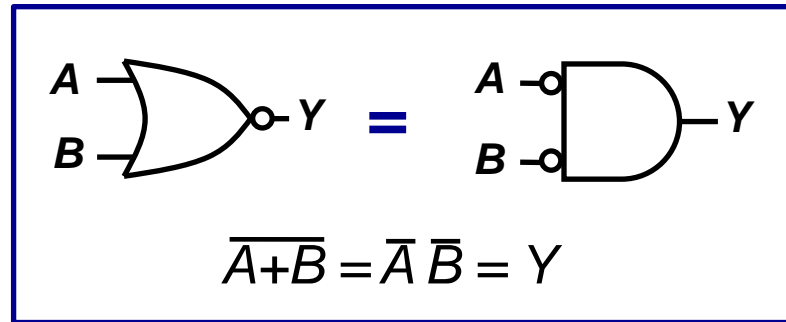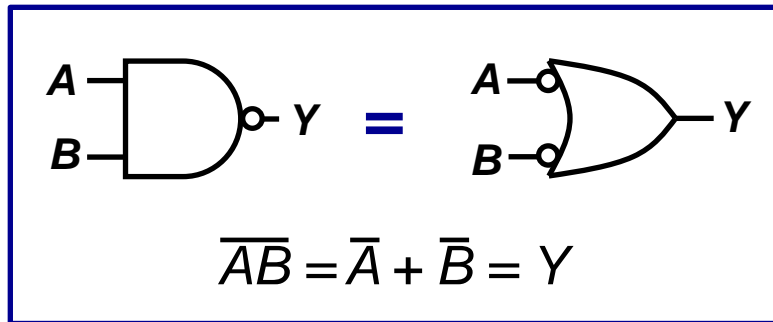The law shows that these gates are equivalent



Important law. For CMOS (Complementary metal–oxide–semiconductor), **NAND** and **NOR** gates are preferred over AND and OR gates, and are also universal (any other gates can be constructed using e.g., NAND).

But how can we know  
that this theorem is  
true?



**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo



# Boolean Algebra (4/4)

## Proof by Perfect Induction

Perfect Induction = Proof by Exhaustion = Proof by Cases

**Prove the De Morgan's Theorem for three variables**

$$\overline{ABC} = \bar{A} + \bar{B} + \bar{C}$$

Proof by **perfect induction**.  
Exhaustively show all cases  
in a truth table.

Note that these two  
columns are equal

A	B	C	$\overline{ABC}$	$\bar{A} + \bar{B} + \bar{C}$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0



## Part II

# Building Blocks: Multiplexers, Decoders, and Adders



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.


**Part I**  
Gates and  
Boolean Algebra



**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo

# Abstractions in Computer Systems

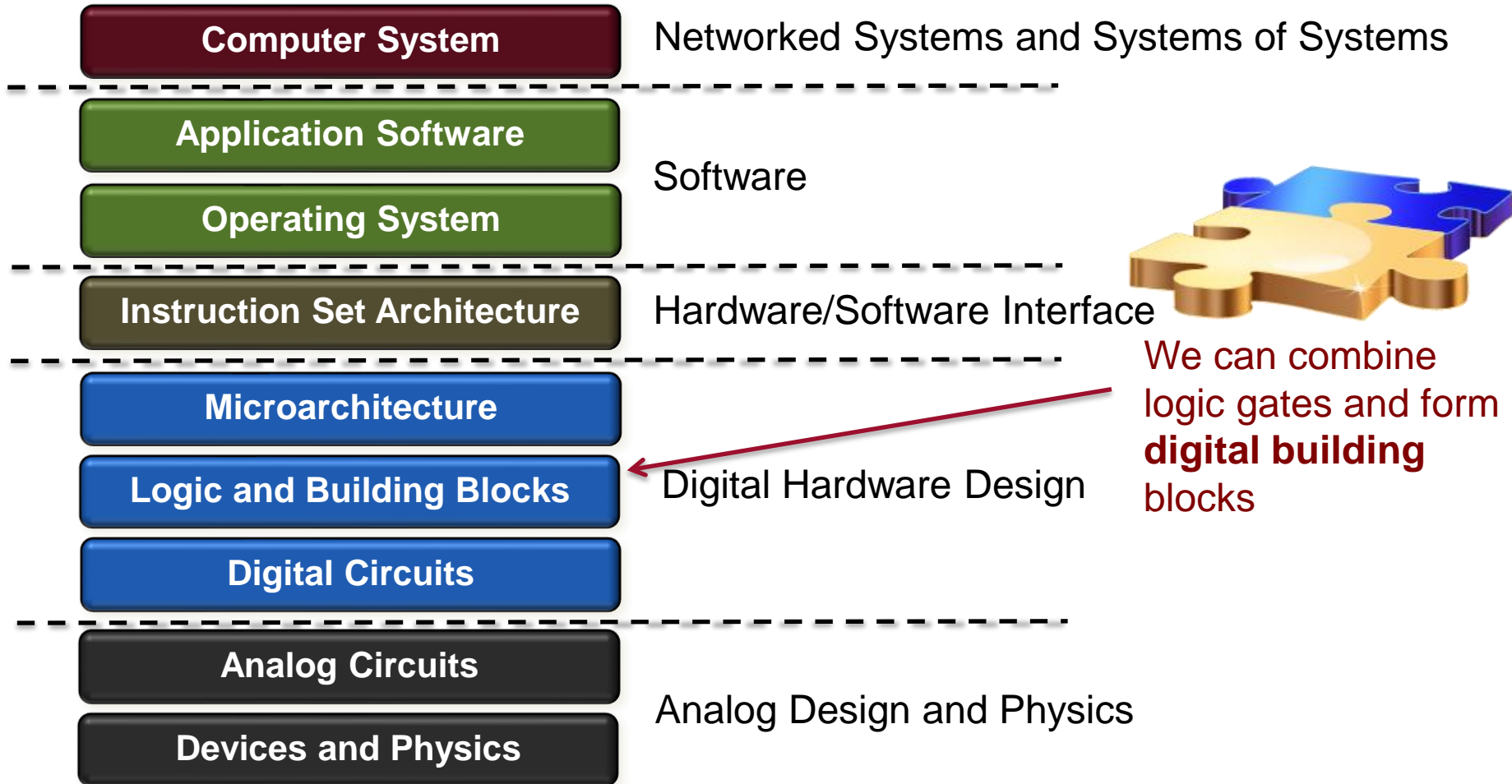

# Combinational Blocks (1/3)


## Multiplexers

What is this?


S	D1	D0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

It's a **2:1 Multiplexer**.

2 bits for the data input

 

 The control signal **S** selects which input bit that is sent to the output.




One possible implementation. Convince yourself of its correctness!

# Combinational Blocks (2/3)
 
## Multiplexers

A **multiplexer** can be seen as a simple switch, selecting which signal that should pass through the block.




**4:1 multiplexer** (4 inputs, 1 output).

 **What is the output signal  $Y$  for the 4:1 multiplexer with these inputs?**

$D0 = 1, D1 = 0, D2 = 1, D3 = 0,$   
 $S1 = 1, S0 = 0$  Answer:  $Y = 1$




A 4:1 multiplexer can be defined hierarchically.



# Combinational Blocks (3/3)
 
## Decoders

A **decoder** has  $N$  inputs and  $2^N$  outputs.  
Asserts exactly one output.



**2:4 decoder** (2 inputs, 4 output).

$A1$	$A0$	$Y3$	$Y2$	$Y1$	$Y0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0




Note that only one signal is 1 on each row. This is called **one-hot**.



# Arithmetic Circuits and Numbers (1/7)
 
## Half and Full Adders

A **half adder** has a *carry out* signal.




How can we add bigger numbers?

Idea: Chain adders together...

A	B	S	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



 A **full adder** has both *carry out* and *carry in* signals.




C <sub>in</sub>	A	B	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Exercise:**  
Complete the truth table

# Arithmetic Circuits and Numbers (2/7)
 
## Carry Propagate Adders

An N-bit **carry propagate adder (CPA)** sums two N-bit inputs.




Three common implementations of CPAs are:

- **Ripple-carry adder**  
Simple but slow.
- **Carry-lookahead adder**  
*Faster, divides into blocks.*
- **Prefix adder**  
Even faster. Used in modern computers.




### 32-bit ripple-carry adder

 


 
# Arithmetic Circuits and Numbers: Remember this circuit?



Written another way:


$$\begin{array}{r} A_{1..0} = \quad "01" \\ B_{1..0} = + \quad "01" \\ \hline Y_{1..0} = \quad "10" \end{array}$$

**A 2 bit adder! (without a carry-out for the second bit)**

# Arithmetic Circuits and Numbers (7/7)

 
## Subtract

Subtract is simple to implemented with a **carry propagate adder (CPA)**:  
Invert input signal B and set  $C_{in} = 1$ .



 **Note that setting carry in to 1 adds 1 to  $A + B$ .**


We can easily create a circuit where  
 $K = 0$  results in  $A + B$  and  
 $K = 1$  results in  $A - B$



In lecture 9, we will generalize this idea into an **Arithmetic/Logic Unit (ALU)**, one of the main components of a processor.

# Part III

## Logisim Demo

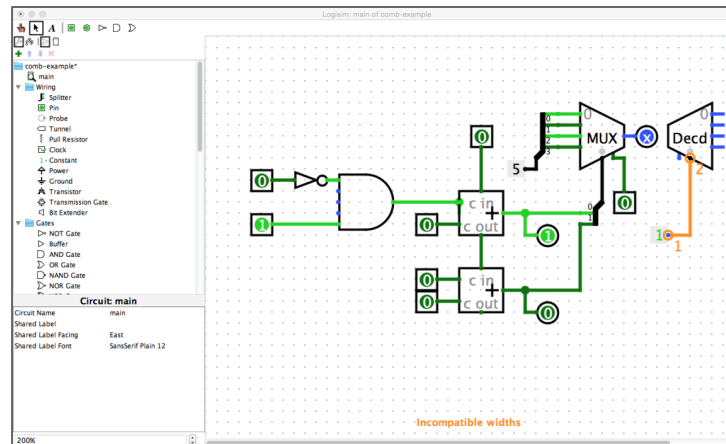

**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo


# Logisim

Free graphical digital circuit simulator.  
Used in the LD-LAB and in LAB4.


**Graphical Model Canvas**  
Both for construction and simulation

**Explorer Pane**  
Building blocks  
and gates

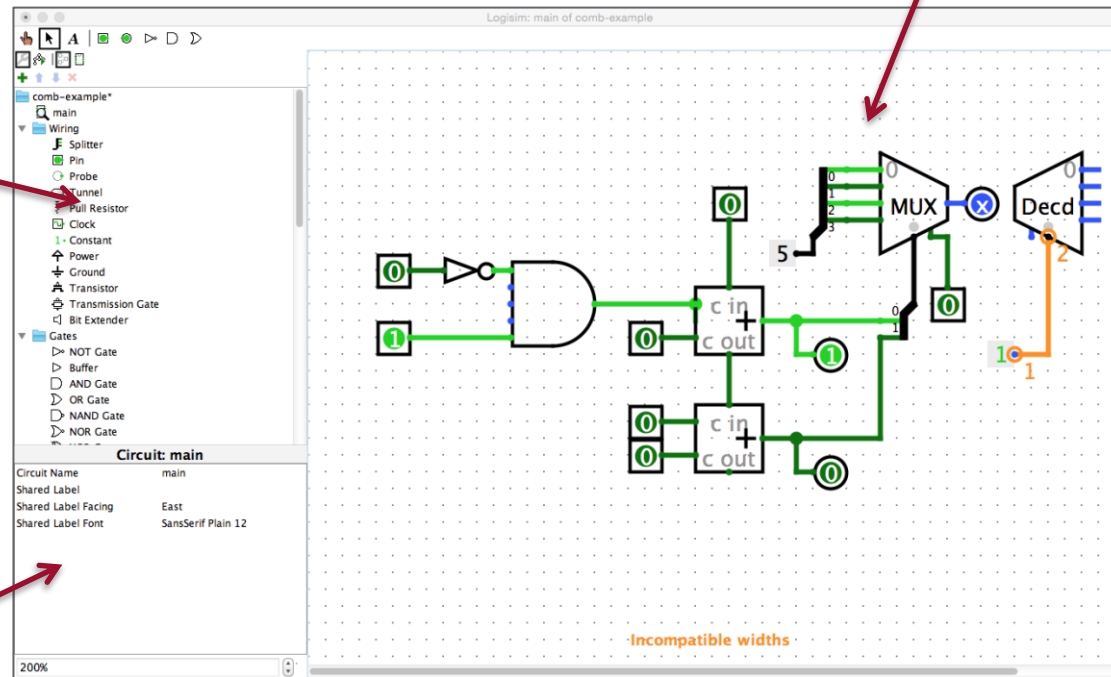
**Attribute Table**  
Configure  
different  
components



# Some Different Notations in Logisim

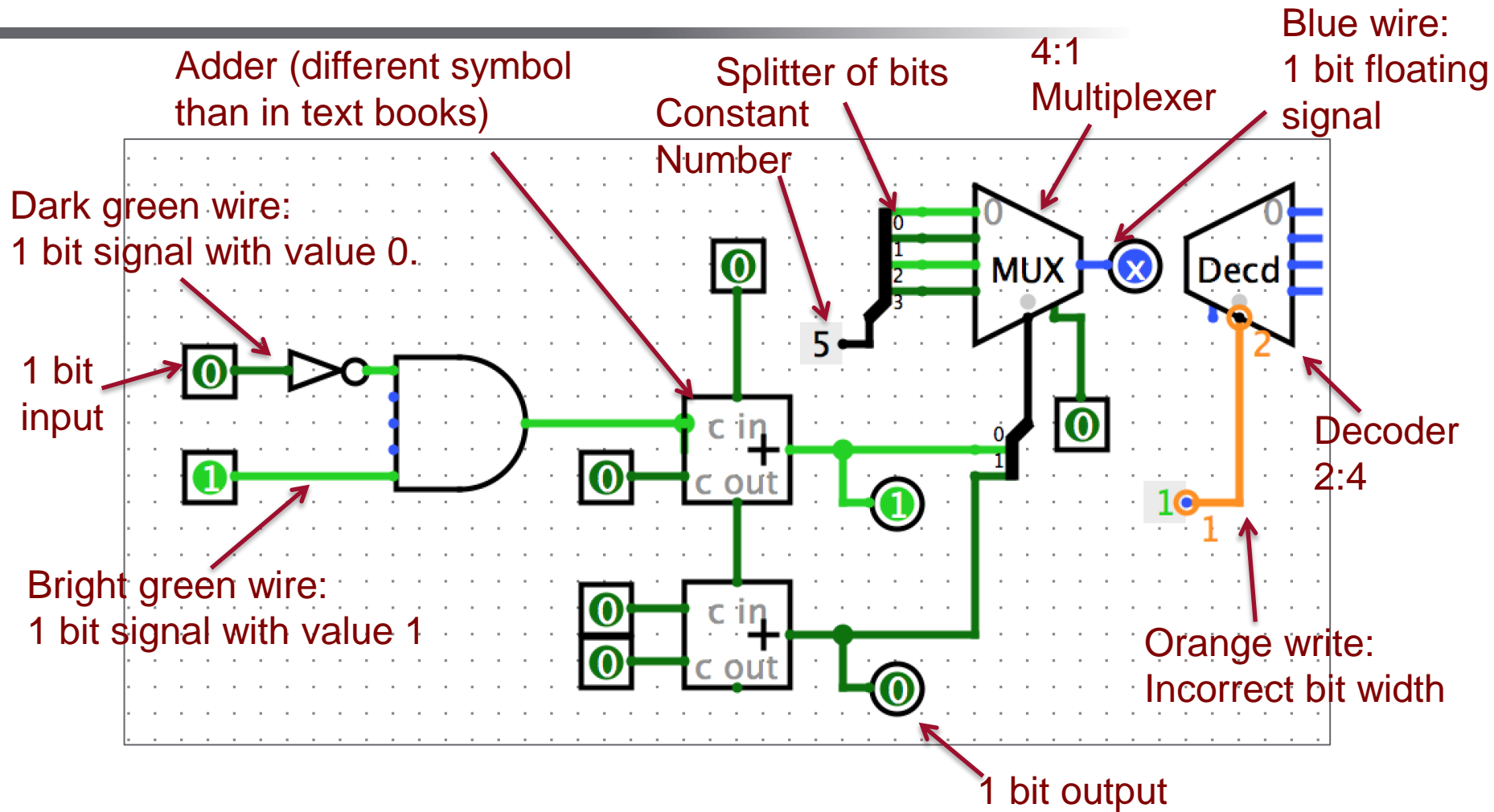

# Hardware Description Languages

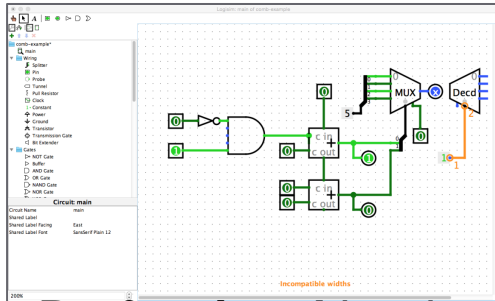

**Logisim** is a simple graphical design and simulation environment for *educational purposes*.

For those who are interested, see Harris & Harris (2012), chapter 4. This is not part of the course.

**Professional** hardware designers work in textual Hardware Description Languages (HDL).

The two most commonly used HDLs in industry are:

- **Verilog/System Verilog**. Used a lot in USA/Japan. C-like syntax.
- **VHDL**. Used more in Europe. Ada-like syntax.

It also exist recent domain-specific languages (DSLs) for hardware design. Ex. **Chisel** from UC Berkeley (embedded in Scala). Also, there are tools that convert from C-code directly to Hardware; these are called **High-Level Synthesis** tools and are becoming very popular.

# We will soon finish!




**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo



# Reading Guidelines

 

## Module 3: Logic Design

### Lecture 7: Combinational Logic Design

- H&H Chapters 1.5, 2.1-2.4, 2.6, 2.8-2.9

### Lecture 8: Sequential Logic Design

- H&H Chapters 3.1-3.3 (not 3.2.7), 3.4.1-3.4.3, 5.2.1-5.2.2, 5.5.5

## Reading Guidelines

See the course webpage  
for more information.

**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo



# Summary

## Some key take away points:

- **Combinational logic design:** Output is directly dependent on input. There is no memory.
- Main components to remember: **multiplexer, decoder, and adder.**
- **Next lecture** is about **sequential logic design**; circuits with memory.



**Thanks for listening!**

**Part I**  
Gates and  
Boolean Algebra

**Part II**  
Building Blocks: Multiplexers,  
Decoders, and Adders

**Part III**  
Logisim  
Demo