

Exercises 3

Logic Design

Computer Organization and Components / Datorteknik och komponenter (IS1500), 9 hp
(not part of IS1200, but can be used for review)


KTH Royal Institute of Technology
Friday 18th December, 2020

Suggested Solutions

Gates and Boolean Algebra


1.

AND




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR




A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT




A	Y
0	1
1	0

NAND




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

XOR

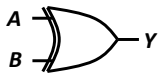

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

2. (a) The truth table is

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(b) The boolean algebra expression is: $\overline{\overline{A} \overline{B}}$.

(c) By applying De Morgan's Theorem, we get $\overline{\overline{A + B}}$, which with the law of involution can be reduced to $A + B$.

3. (a) The truth table is

A	B	C	Y_1	Y_2
0	0	0	1	0
0	0	1	1	1
0	1	0	0	Z
0	1	1	0	Z
1	0	0	0	Z
1	0	1	0	Z
1	1	0	1	0
1	1	1	1	1

(b) The tristate buffer passes through the input data if the enable signal is true, else the output signal is said to be *floating*. This is indicated in the truth table with character Z. When a signal is floating, it means that the signal has high impedance, that is, giving similar behavior as if the wire was disconnected.

4. (a) $\overline{S} \overline{A} B + \overline{S} A B + S A \overline{B} + S A B$

By commutativity, change the order in the first two terms

$$\overline{S} B \overline{A} + \overline{S} B A + S A \overline{B} + S A B$$

By using the law of distributivity, we can break out the terms

$$\overline{S} B (\overline{A} + A) + S A (\overline{B} + B)$$


Not that we can do this since we can interpret $\overline{S} B$ as one symbol. Using the dual theorem for complements we get

$$\overline{S} B \cdot 1 + S A \cdot 1$$

Finally, using identity, we get


$$\overline{S} B + S A$$

(b) A possible circuit is as follows

 

Multiplexers, Decoders, and Adders

 
5. (a) A 2:1 multiplexer looks as follows



- (b) A truth table can be written as follows. Note how the symbol ? for “don’t care” means that it does not matter if this value is 1 or 0: it gives the same output anyway.


S	A	B	Y
0	?	0	0
0	?	1	1
1	0	?	0
1	1	?	1

- (c) A possible circuit is as follows

 

- (d) It is exactly the same circuit! Note also how the truth table in exercise 4 compares with the one above.

6. (a) A 3:8 decoder looks as follows

 


- (b) Truth table

$A1$	$A0$	$Y3$	$Y2$	$Y1$	$Y0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Note that only one output signal is true at the same time.

- (c) For the expression $X:Y$ (for instance $X = 2$ and $Y = 4$ in a 2:4 decoder), symbol X means the number of input bits, and Y the number of output bits. Note also the relationship $Y = 2^X$.


(d) A possible solution:

 

 
7. The following multiplexor shows that the output data signal has a 8-bit bus width. As a consequence, the input data bus width must also be 8-bit. Hence, we only need to specify one of the signals, either the input or the output.



 8. The following circuit implements a 6-bit ripple-carry adder. Multiplication by 3 is done by shifting the input to the left by 2, and then subtracting the input value.



 9. One possible solution for a 4-bit equality comparator.




Latches, Flip-Flops, Registers, and Register Files

10. An SR latch can be described with the following truth table.


S	R	Q	\overline{Q}
0	0	Q_{pre}	\overline{Q}_{pre}
0	1	0	1
1	0	1	0
1	1	0	0

11. (a)

 

- (b) A D Flip-Flop is edge triggered and not level-triggered, as in the case of the D latch. The SR latch does not have a data input, as both D Flip-Flops and D latches have.

- (c)

 

12. (a) At the start, $Y_1 = 0 \times 3$ and $Y_2 = 0 \times 5$, that is, the initial values of the registers. Note that each of the registers hold a 8-bit value. After the first rising edge, the registers read the value that is available on the left hand side. R1 then receives value 0×8 because it receives the sum of value Y_2 and $A = 0 \times 3$. R2 just receives the value from Y_1 . Hence, after the first rising edge $Y_1 = 0 \times 8$ and $Y_2 = 0 \times 3$. After the second clock cycle, we have $Y_1 = 0 \times 6$ and $Y_2 = 0 \times 8$, and after the third $Y_1 = 0 \times B$ and $Y_2 = 0 \times 6$.
- (b) In this exercise, it is important to notice that the XOR gate works as an inverter, since $B = 255$ means that all bits are set to one. Convince yourself that XORing with value one inverts a signal. Since the carry in signal to the adder is 1, the circuit will perform a subtraction of value 2 in each iteration. At start, $Y_1 = 0 \times 10$ and $Y_2 = 0 \times 8$. After the first rising edge $Y_1 = 0 \times 6$ and $Y_2 = 0 \times 10$. After the second clock cycle, we have $Y_1 = 0 \times E$ and $Y_2 = 0 \times 6$, and after the third $Y_1 = 0 \times 4$ and $Y_2 = 0 \times E$.
13. (a) A register is a memory that is updated at a clock edge. A register also has a memory, and it is also updated at a clock edge. However, a register file is a simple addressable memory, where you specify an address for where you should read and write data. A register has no address, and the whole register is updated at the clock edge. Both a register file and a register can either be triggered on the raising or falling edge.
- (b) The register file has two read ports and one write port.
- (c) Each data item is 16 bits large and the register file can address $2^4 = 16$ data items. Hence, the total number of bits that can be stored in this register file is $16 * 16 = 256$ bits.
- (d) $RD_1 = 0 \times 22$ and $RD_2 = 0 \times e7$. The new known state is $\{0 \times 3 \mapsto 0 \times 53, 0 \times a \mapsto 0 \times 22, 0 \times 9 \mapsto 0 \times e7\}$