



Computer Hardware Engineering (IS1200)

Computer Organization and Components (IS1500)


Spring 2021

Lecture 9: ALU and Single-Cycle Processors

Daniel Lundén

PhD Student, KTH Royal Institute of Technology

 Slides by David Broman (extensions by Artur Podobas), KTH







Course Structure



Module 1: C and Assembly Programming

 


Module 2: I/O Systems

 


Module 3: Logic Design (IS1500 only)

**PROJ
START**

 

Module 4: Processor Design

 

Module 5: Memory Hierarchy



Module 6: Parallel Processors and Programs



Proj. Expo


LE14

Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

Abstractions in Computer Systems

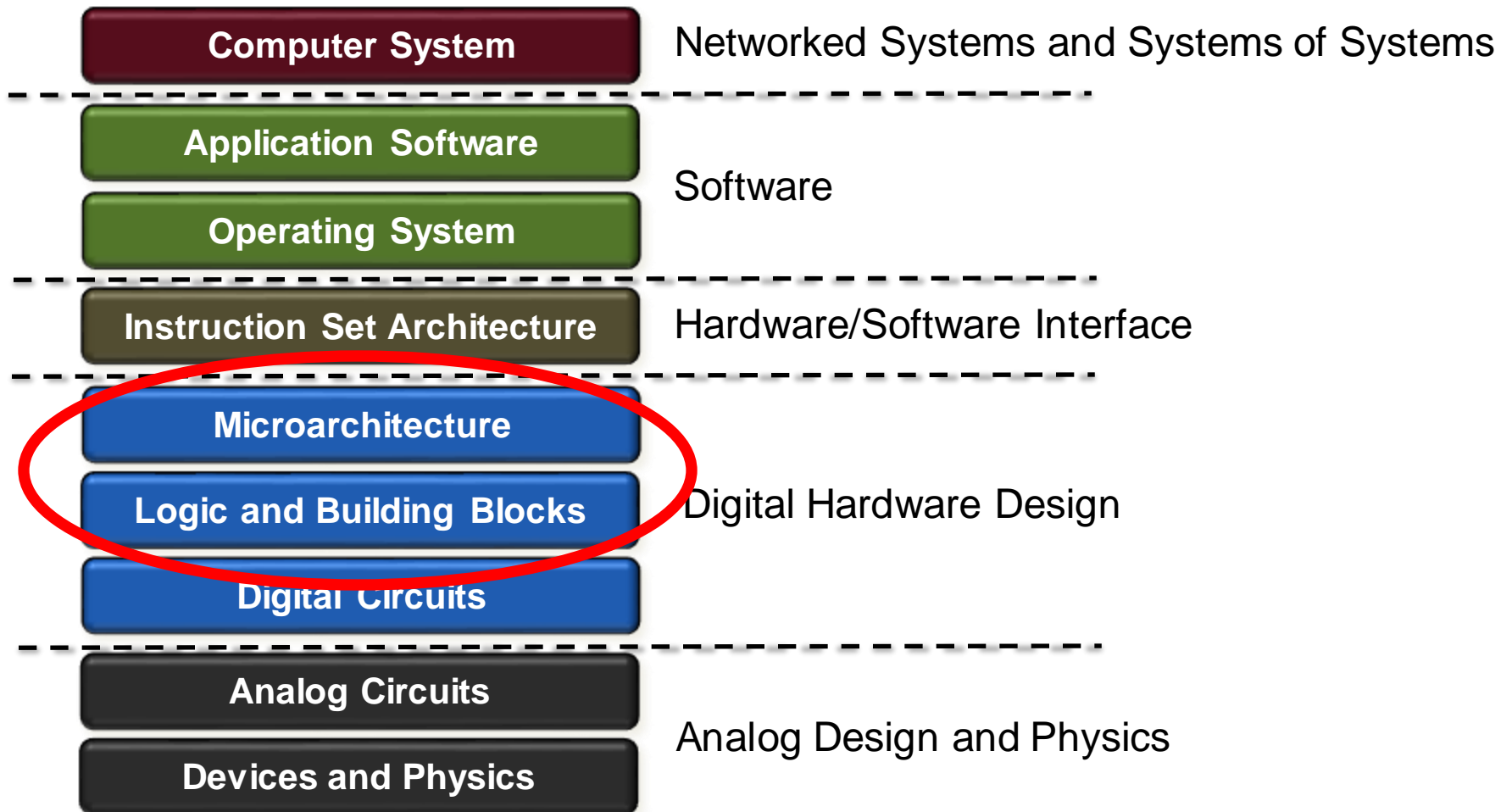

Agenda


Part I

Arithmetic Logic Unit



Part II

Data Path in a Single-Cycle Processor

 

Part III

Control Unit in a Single-Cycle Processor



Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

Part I

Arithmetic Logic Unit



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.





Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

Arithmetic Logic Unit (ALU)

  An **ALU** saves hardware by combining different arithmetic and logic operations in one single unit/element.



Input **F** specifies the function that the ALU should perform

ALUs can have different functions and be designed differently.

ALU symbol: both figures have the same function

An ALU can also include **output flags**, for instance:

- **Overflow flag** (adder overflowed)
- **Zero flag** (output is zero)
- **Negative flag** (if the value is negative)
- **Carry flag** (result of addition)



Part I
Arithmetic
Logic Unit


Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

Arithmetic Logic Unit (ALU)

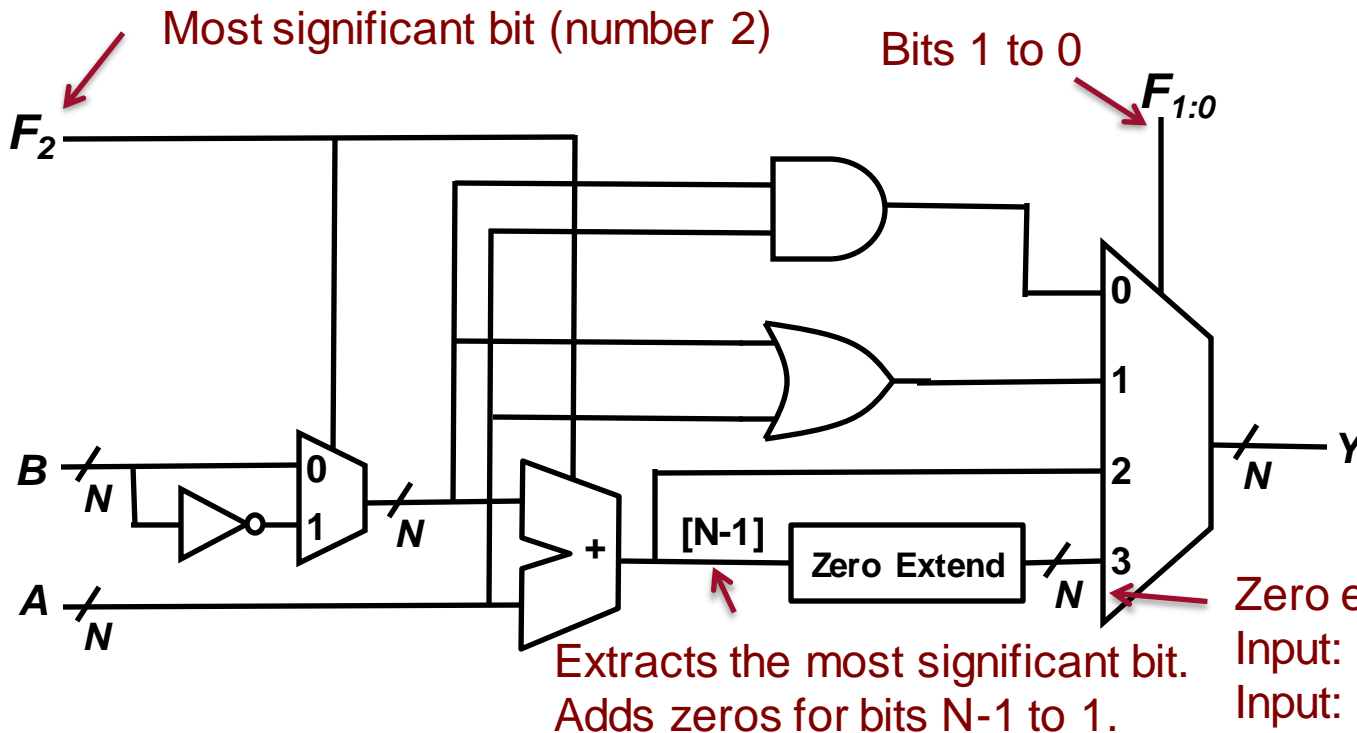Exercise:

Determine the functional behavior for each value of **F**.



$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND !B
101	A OR !B
110	A - B
111	SLT




Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

Part II

Data Path in a Single-Cycle Processor

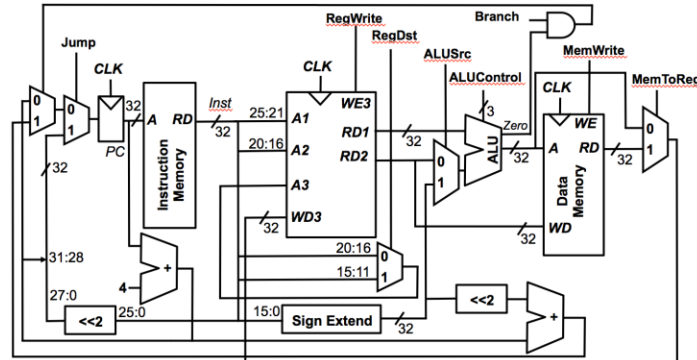


Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.



Data Path and Control Unit

 A processor is typically divided into two parts



Data Path

- Operates on a word of data.
- Consists of elements such as registers, memory, ALUs etc.



Control Unit

- Gets the current instruction from the data path and tells the data path how to execute the instruction.



Instructions

In this lecture, we construct a microarchitecture for a subset of a MIPS processor with the following instructions

R-Type: add, sub, and, or, slt

Arithmetic / logic instructions

Memory instructions

I-Type: addi, lw, sw, beq

Arithmetic
immediate
instruction

Branch instructions


J-Type: j



State Elements (1/3)

Program Counter and Register File

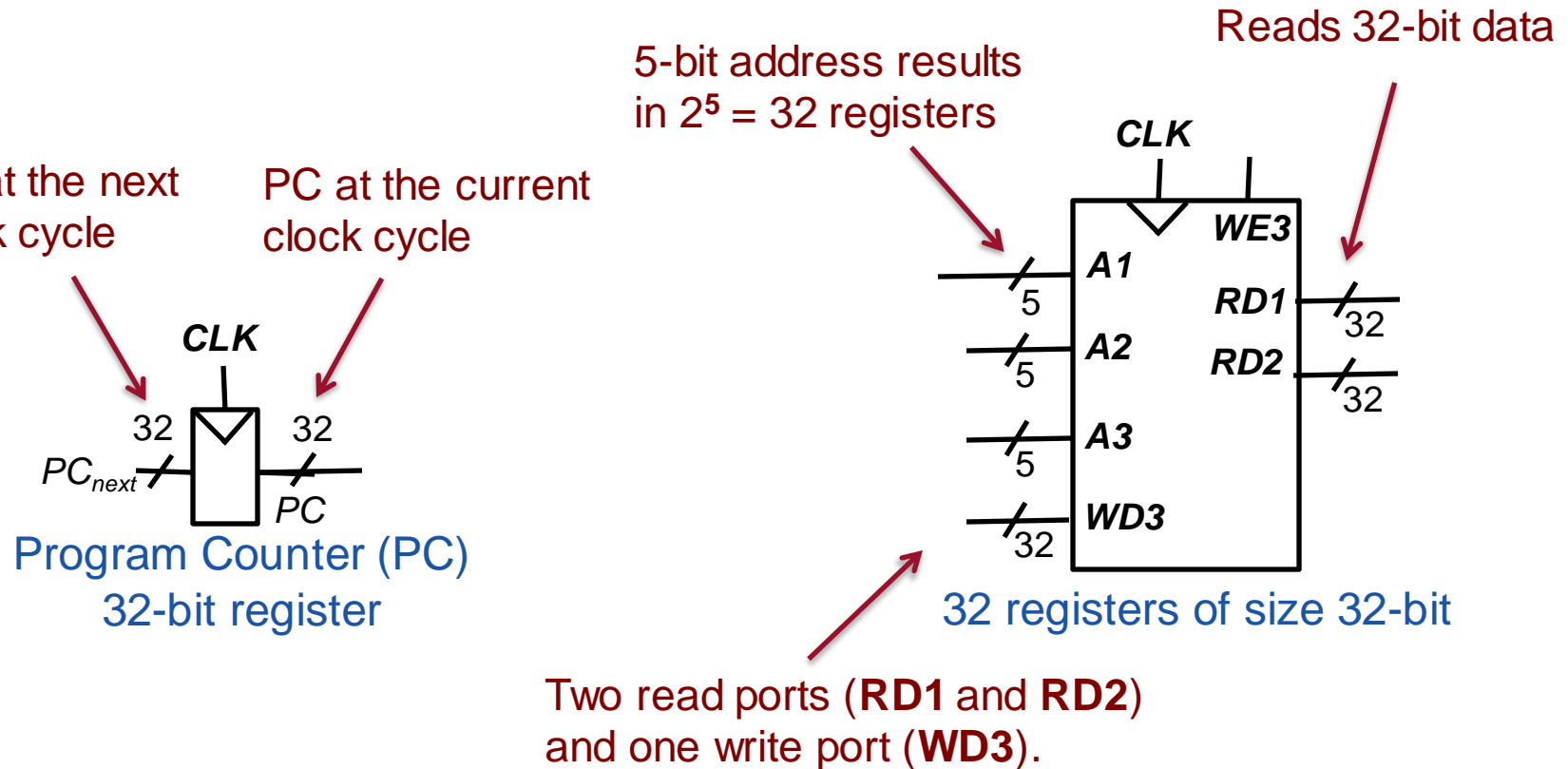The **architectural states** for this MIPS processor are the program counter (PC) and the 32 registers (\$0, \$t0, ... \$s0, \$s1, ... etc.)




State Elements (2/3)

Instructions and Data Memories

32-bit address


Reads 32-bit word of data

 

A simplified instruction memory, modeled as a read-only memory (ROM)

32-bit address

 Writes on the rising clock edge and when write enable (WE) is true



Reads or writes 32-bit word of data

Non-architectural states are used to simplify logic or improve performance (introduced in the next lecture).


State Elements (3/3)

Reading combinationaly, writing at clock edge


All the blocks below **read** *combinationaly*: when the address changes, the data on the read port change after some propagation time.

There is no clock involved.

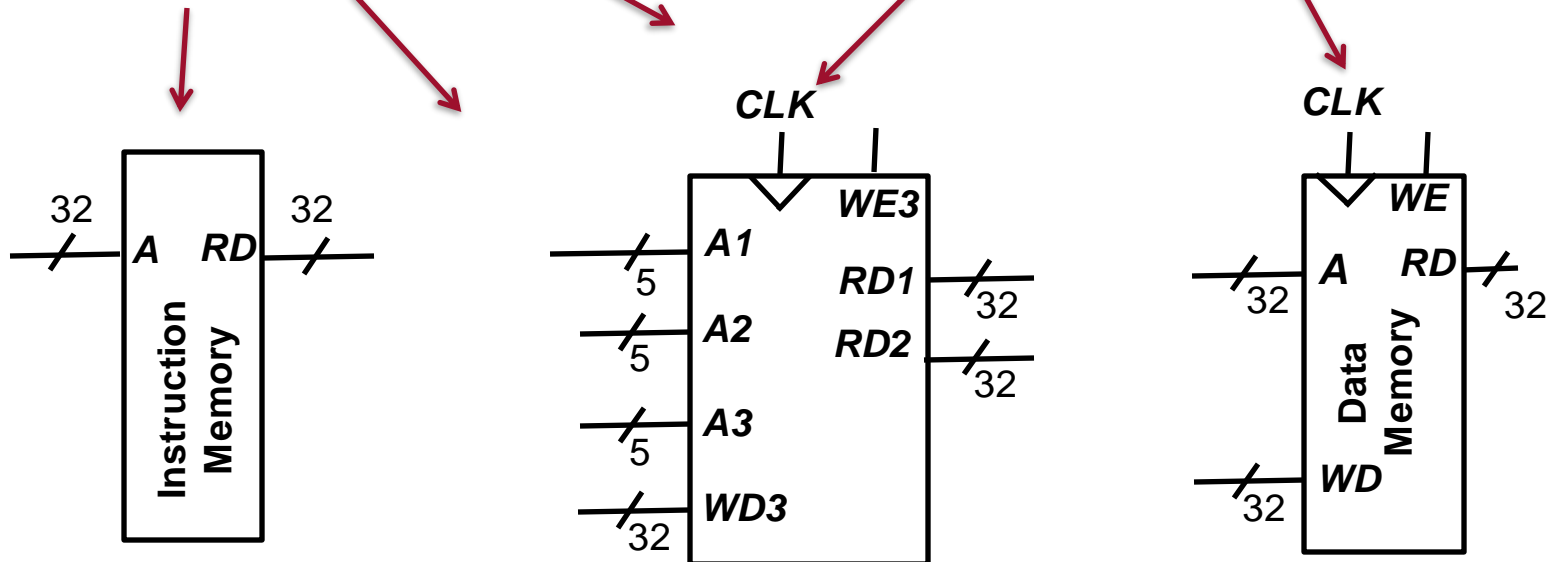The register file and the data memory **write** at the rising clock edge.




Read Instruction from the Current PC

 

First step. Read the instruction at the current PC address.

A 32-bit instruction $Instr$ is **fetched**.

lw instruction – Read Base Address

 


Example

lw \$s0, 4(\$s1)

Read out the base address from the register file. 25:21 cuts out the 5 bits from the instruction.

Base address in rs

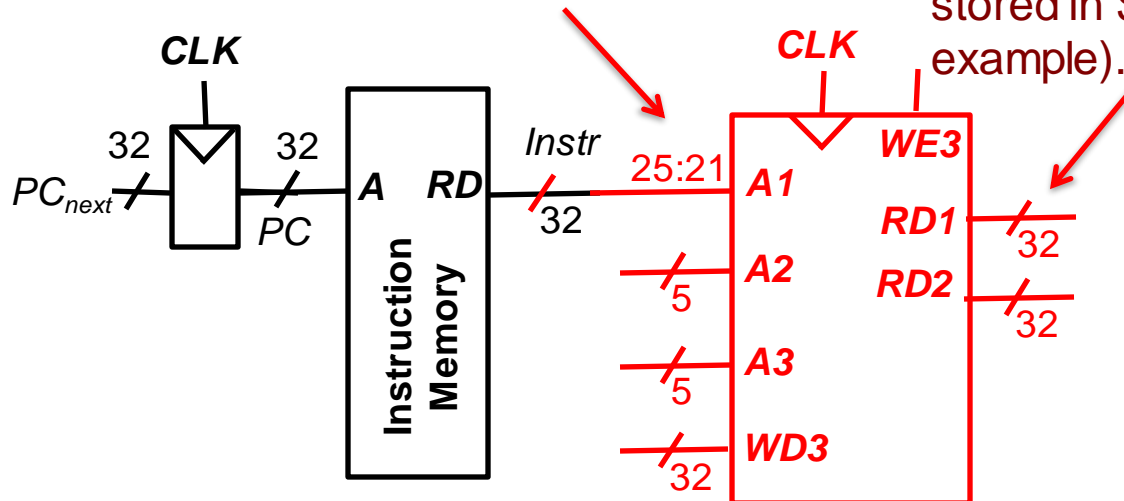
RD1 holds the address stored in \$s1 (in the above example).



Loads the value from memory \$s1+4 and stores the result in \$s0.




lw instruction – Read Offset

 

Example

lw \$s0, 4(\$s1)

The offset is stored in the imm field.

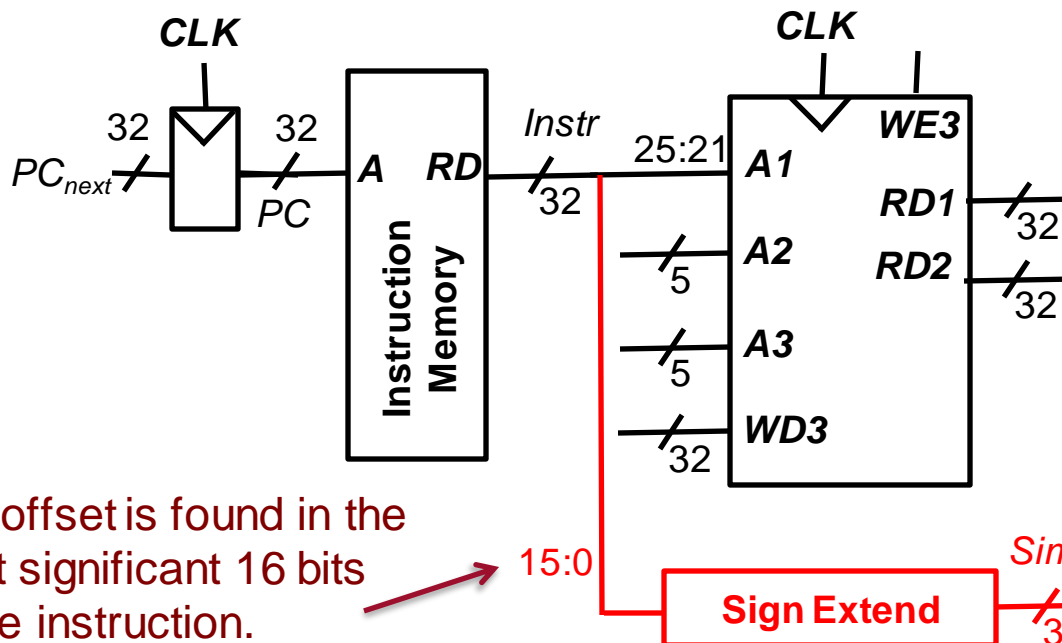


The offset is signed.
Sign extend to 32 bits.

That is:


$$Simm_{15:0} = Instr_{15:0}$$

$$Simm_{31:16} = Instr_{15}$$

lw instruction – Read Data Word

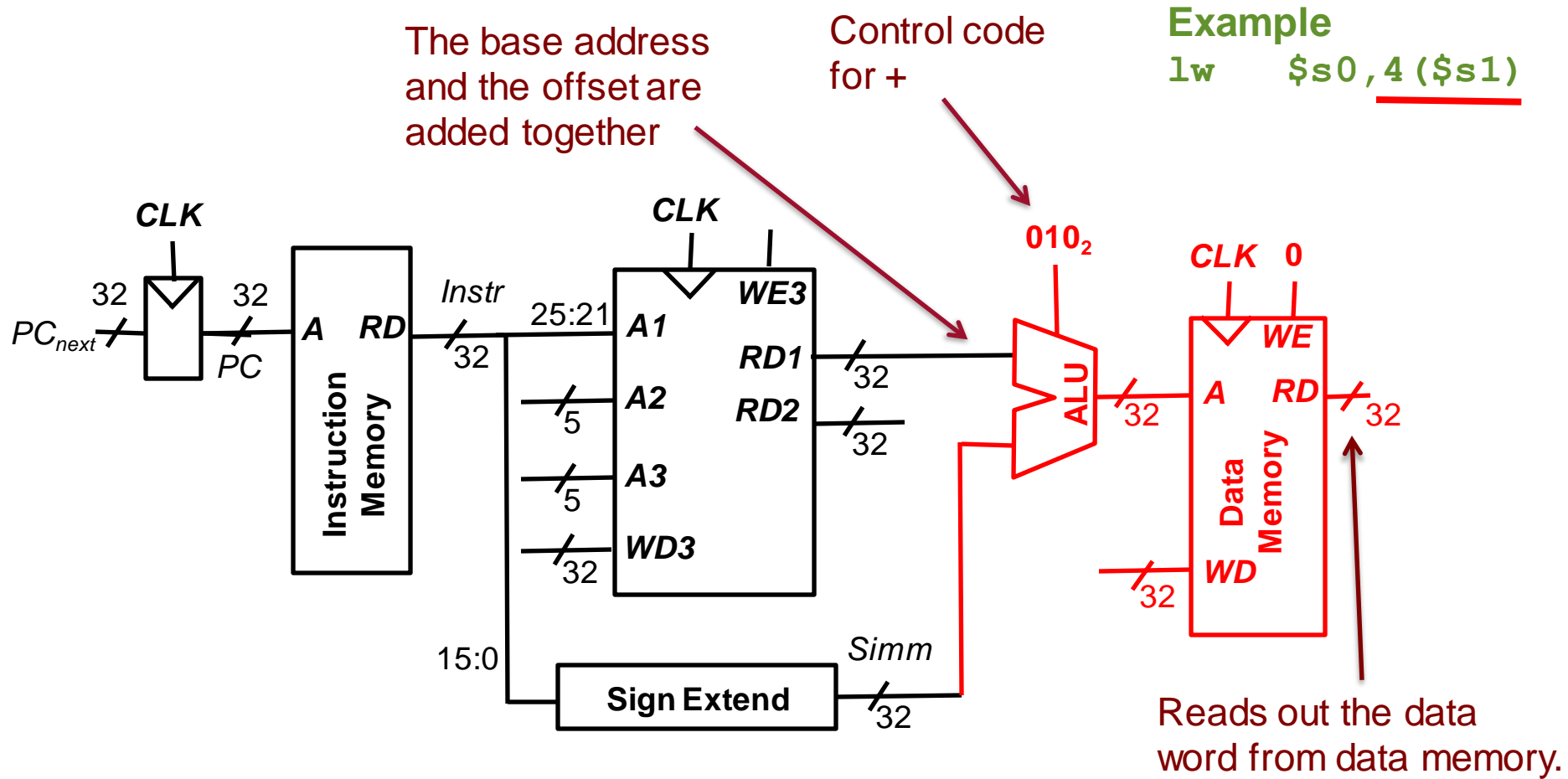


lw instruction – Write Back

 


Example

lw \$s0, 4 (\$s1)

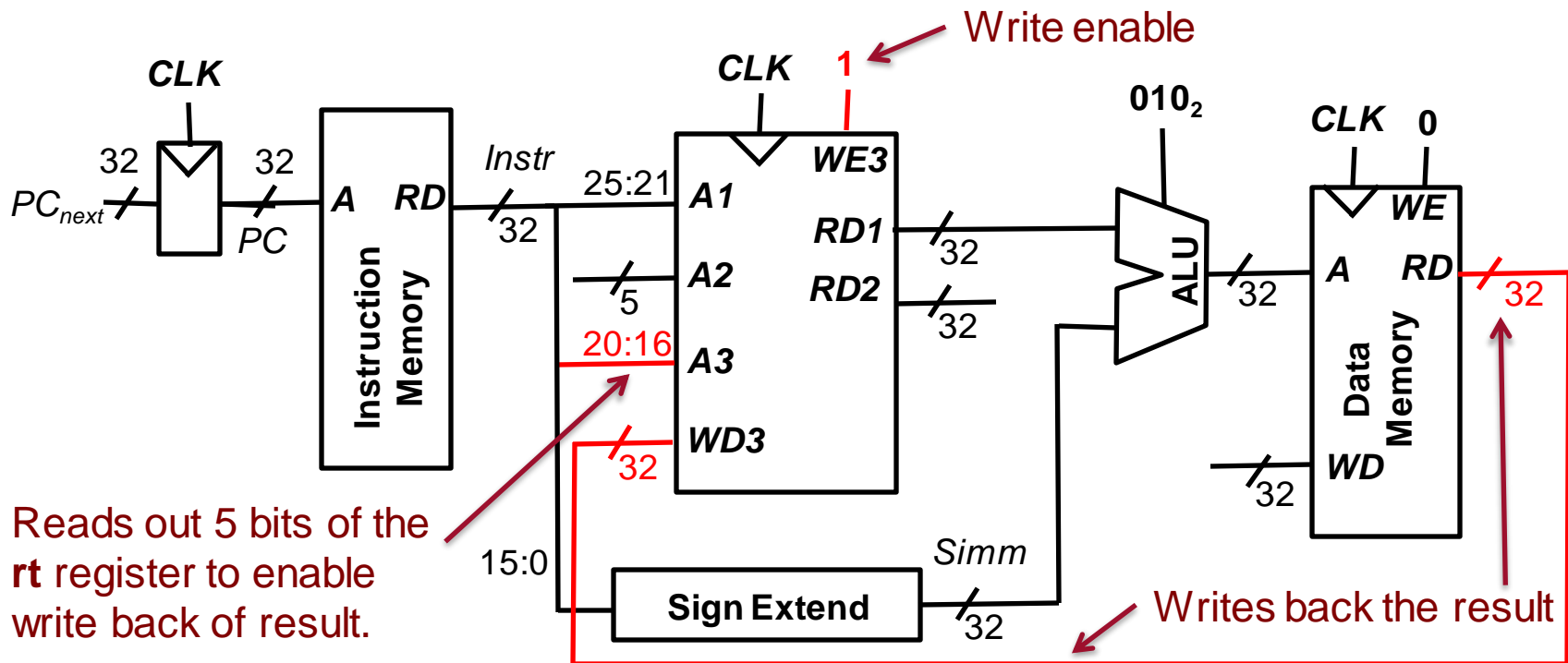


1w instruction – Increment PC

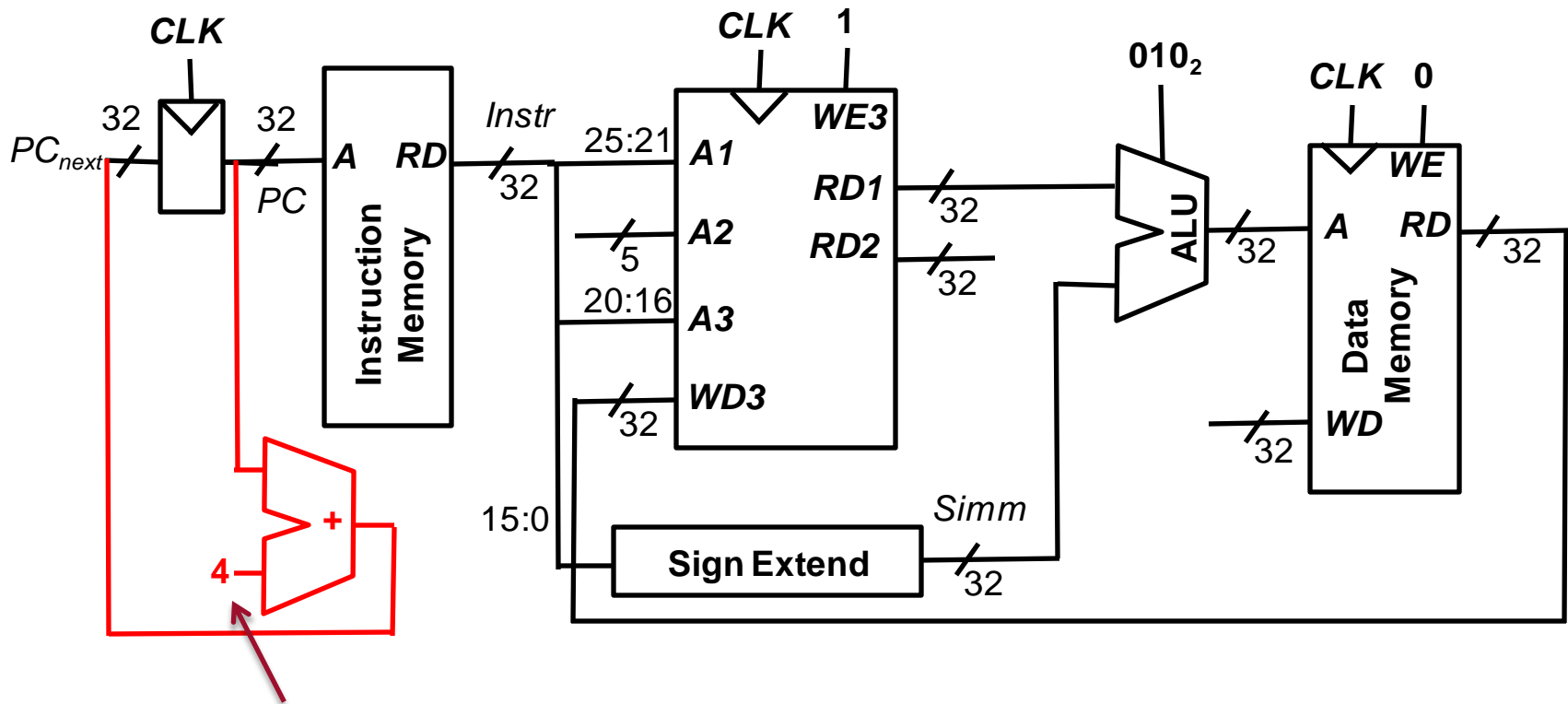

Increment the PC by 4.
(Next instruction is at address PC + 4)

This is the complete data path for the load word (1w) instruction.


1w instruction – Timing

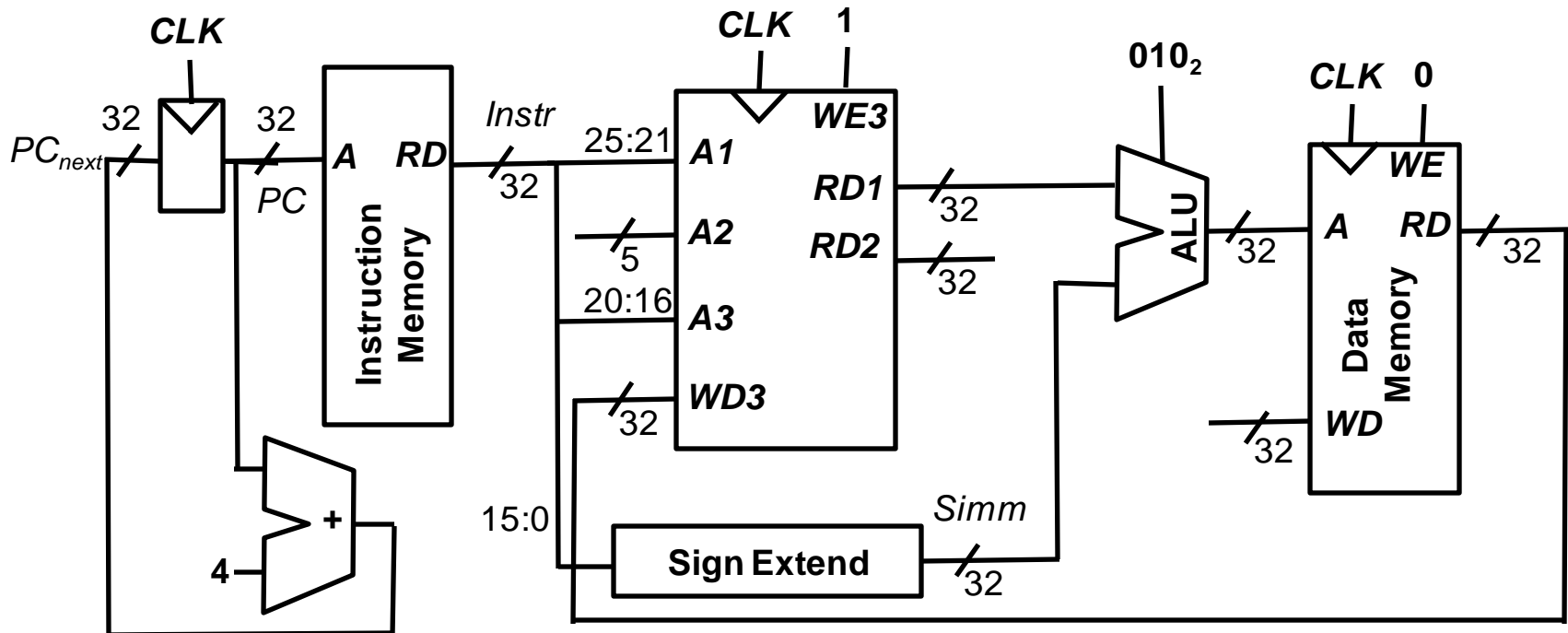

Combinational logic during clock cycle:
read instruction, sign extend, read from
register file, perform ALU operation, and
read from the data memory.

At the rising clock edge:
Write to the register file
and update the PC.

CLK

 

Part I
Arithmetic
Logic Unit



Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

sw instruction – Increment PC

We need to read the base address, read the offset, and compute an address. Good news: **We have already done that!**


Example

sw \$s0, 4(\$s1)

The word to be stored is saved in a register (**rt-field** in the I-type)

Write enable must be false

The data word is stored into the memory

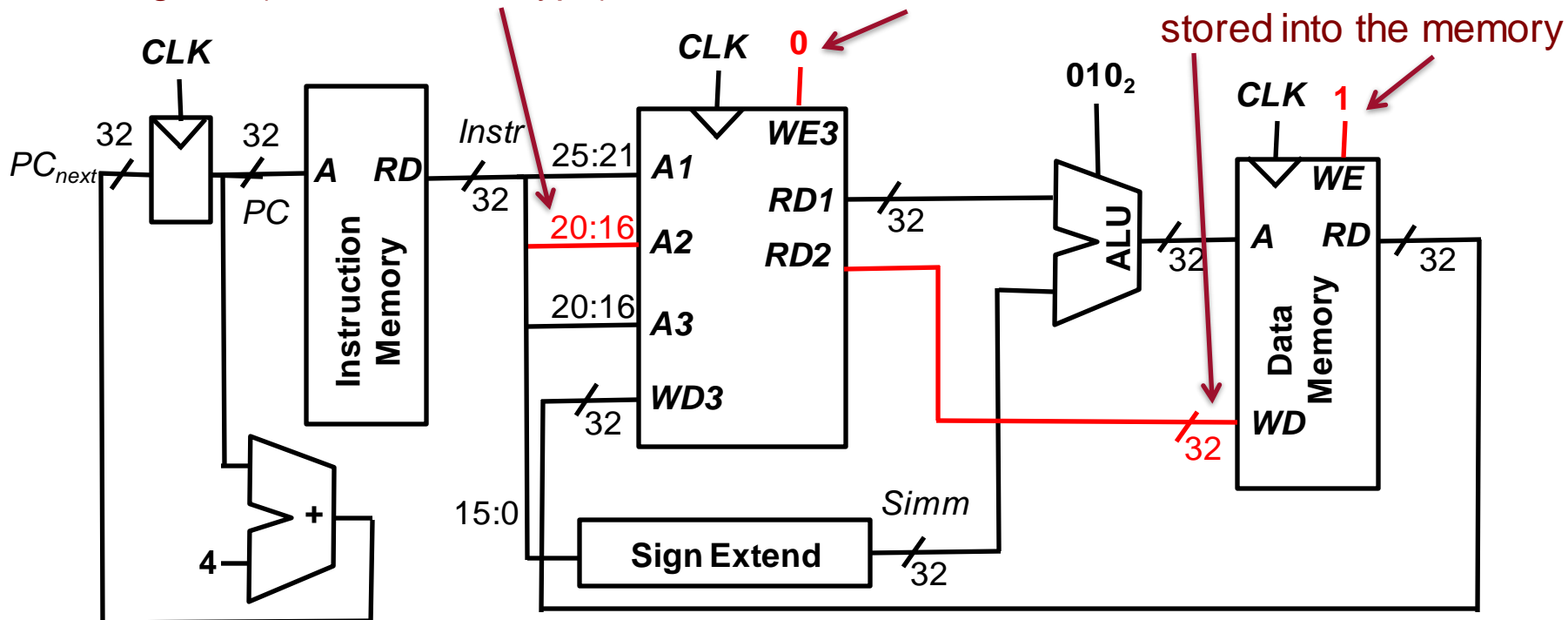

Part I
Arithmetic
Logic Unit




Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor

R-type instructions – Machine Encoding

 
We are now going to handle all R-type instructions the same uniform way. That is, we should handle **add**, **sub**, **and**, **or**, and **slt**.



R-type instructions – ALU Usage

We want to send the second operand to the ALU, but still be compatible with the `lw`-instruction.

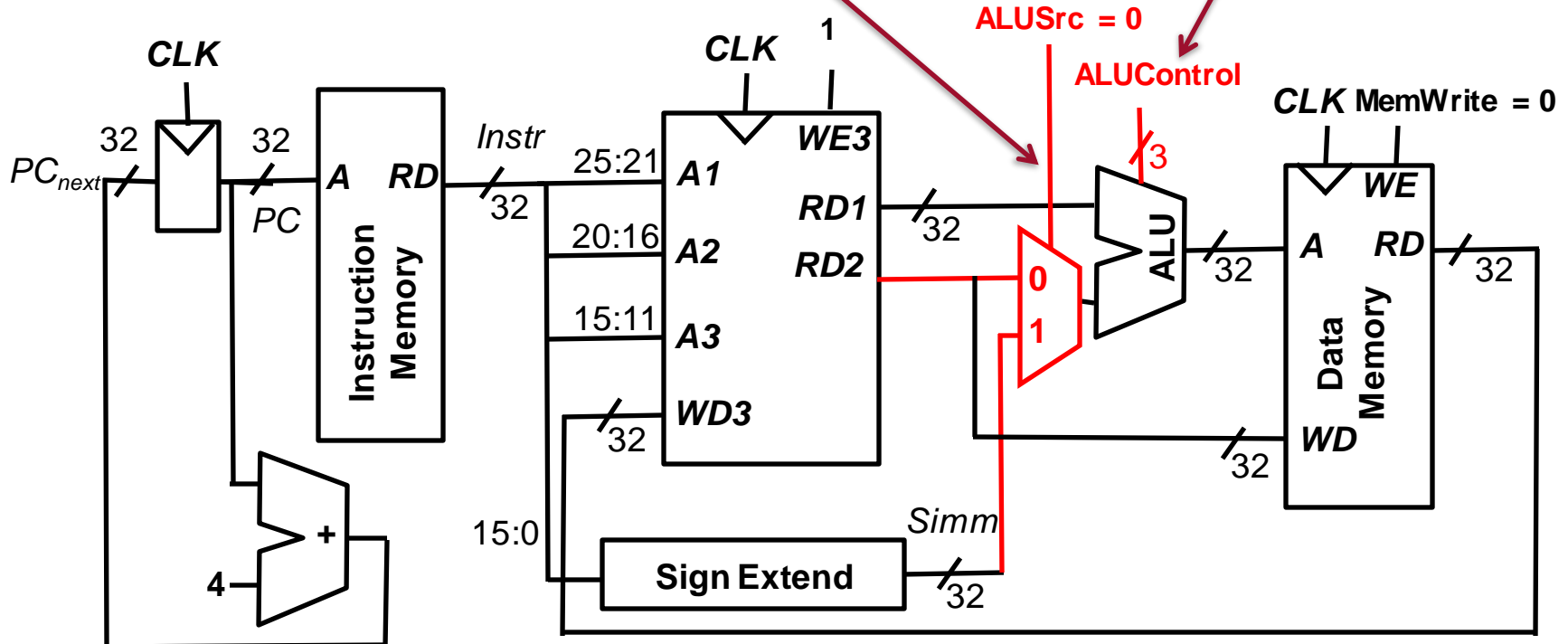
Different ALU control signals for different instructions.



R-type instructions – Write to Register


R-Type instructions write to registers and not to memory.

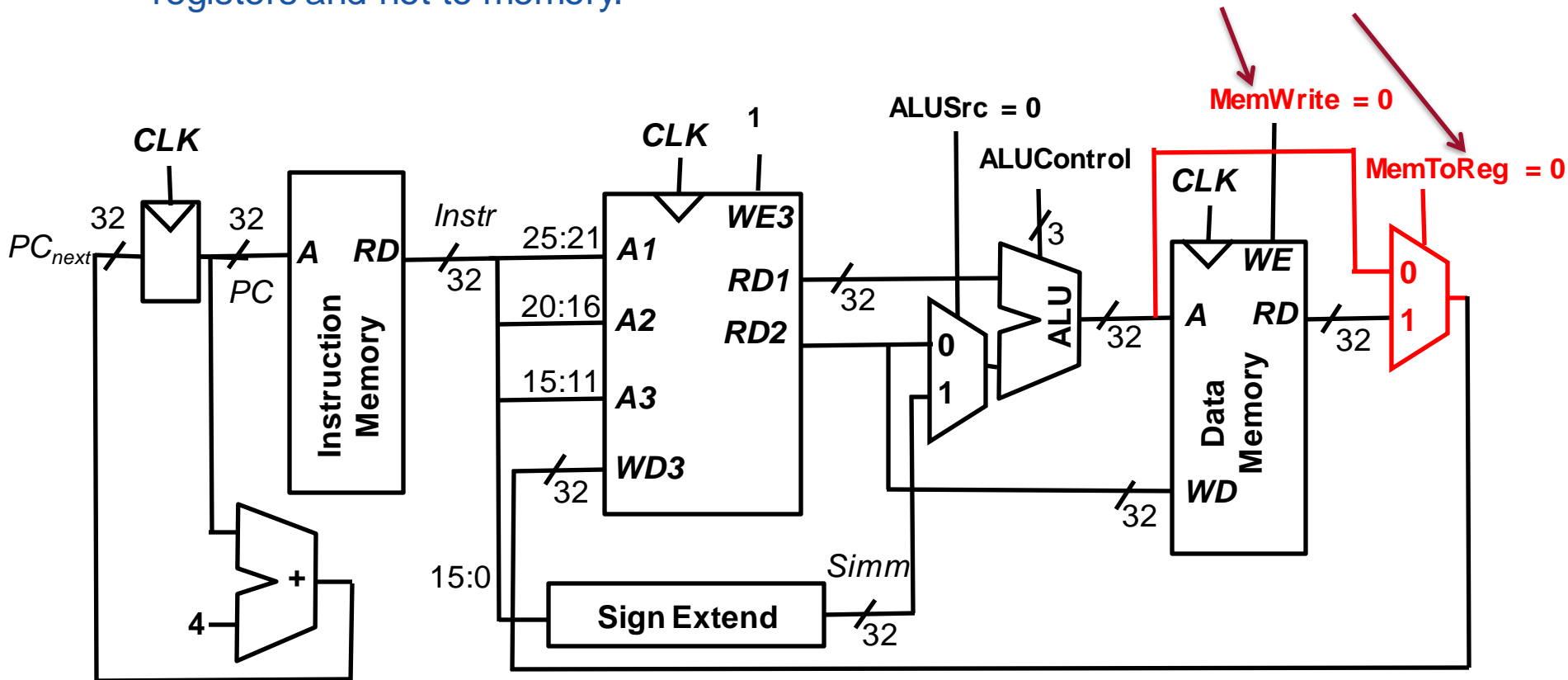Bypass the the data memory if an R-Type instruction



R-type instructions – Machine Encoding


I-Type

 


For the **lw** instruction, the target register is stored in the **rt** field (bits 20:16)

For R-type instructions, the target register is stored in the **rd** field (bits 15:11)

R-Type

 


R-type instructions – Use the rd field

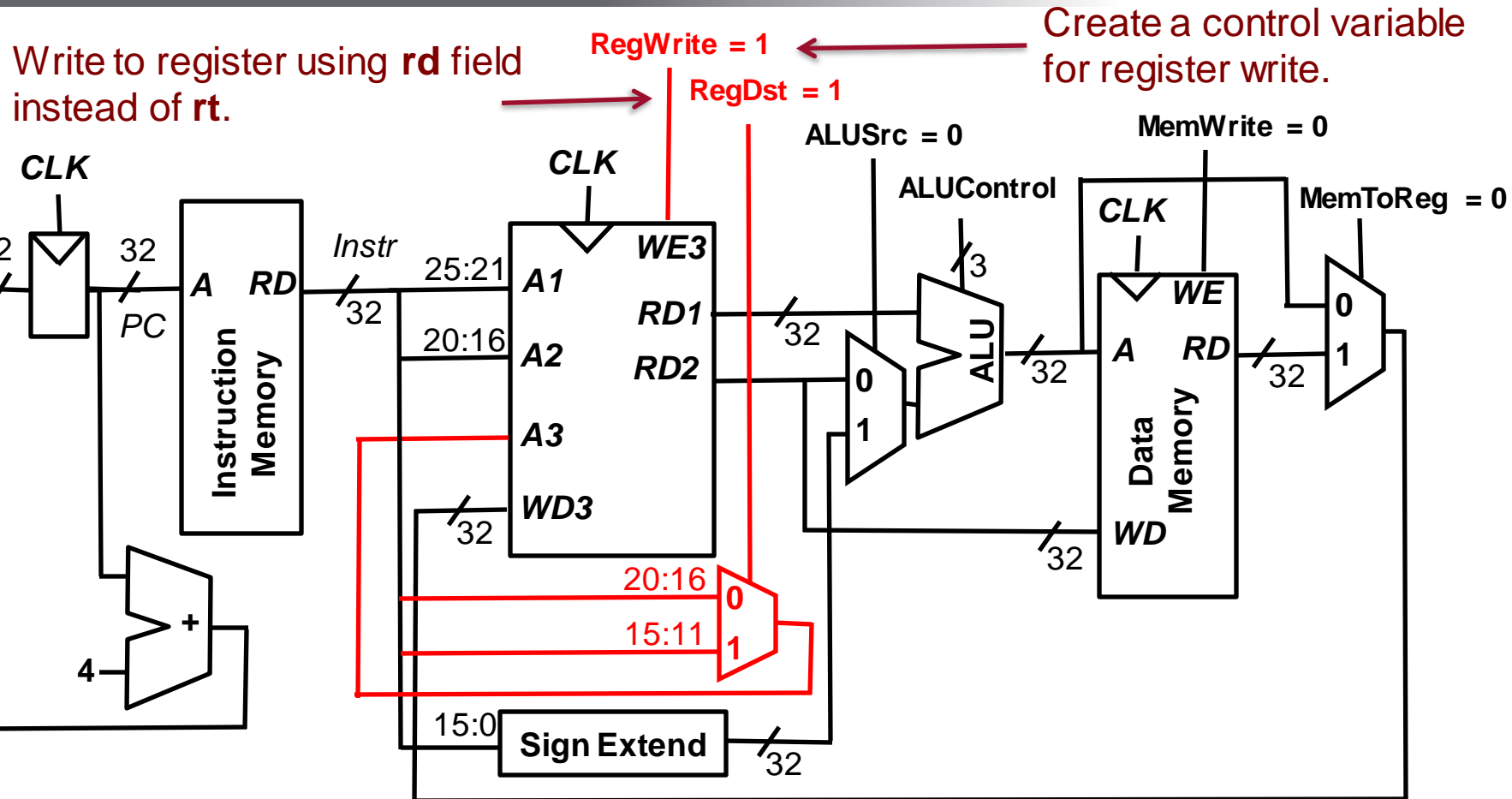

beq instruction – Machine Encoding

 Recall that the **beq** instruction is a branch instruction, encoded in the I-Type.



Recall how to compute the BTA:

$$\text{BTA} = \text{PC} + 4 + \text{imm} * 4$$


Example

beq **\$s0, \$s1, loop**



beq instruction


Compare if equal

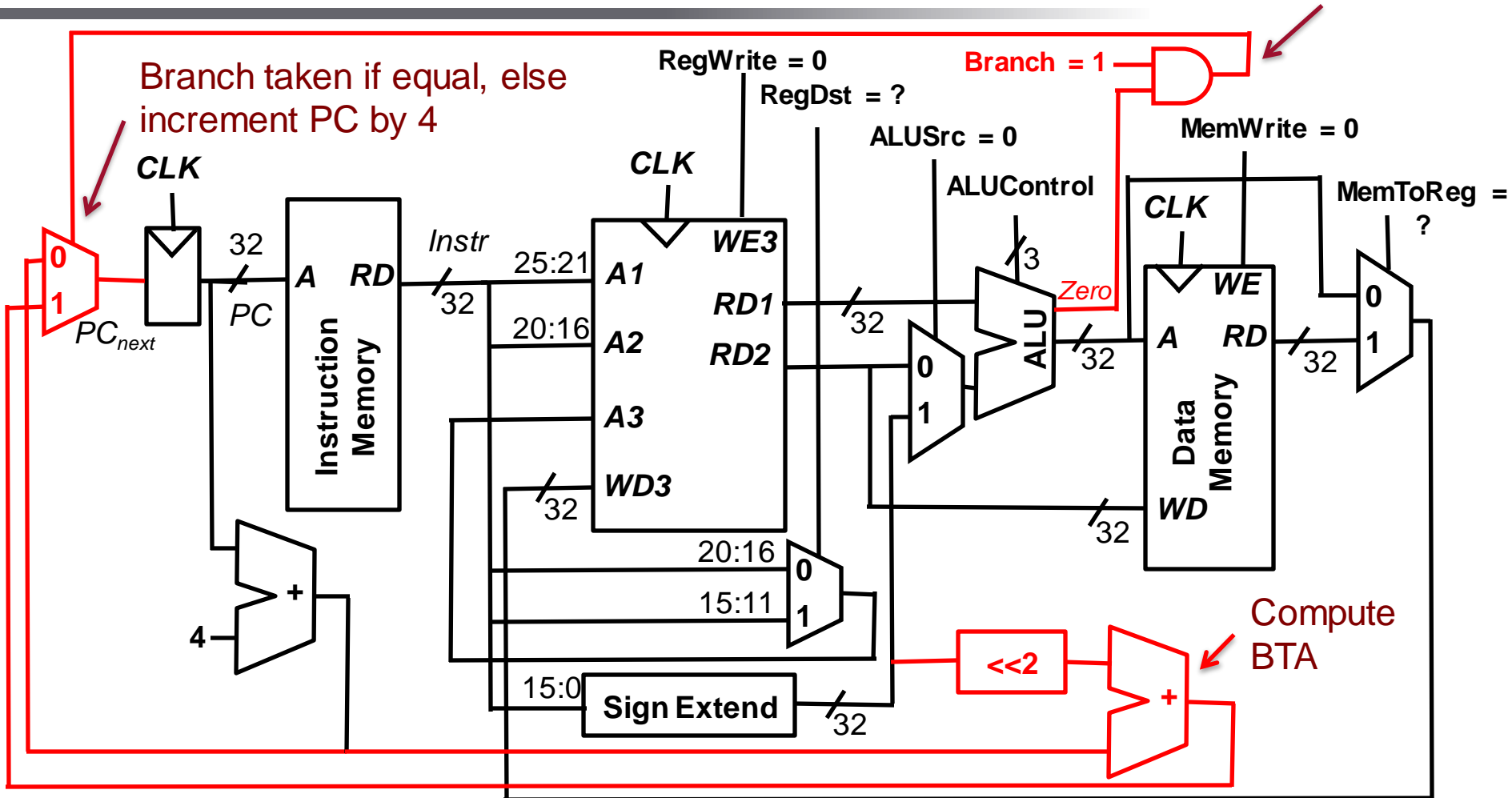

Data Path for Instructions

`add, sub, and, or, slt, addi, lw, sw, beq, j`

Note: we have indirect support for `addi` (with sign extension), but `ori` would need additional logic.

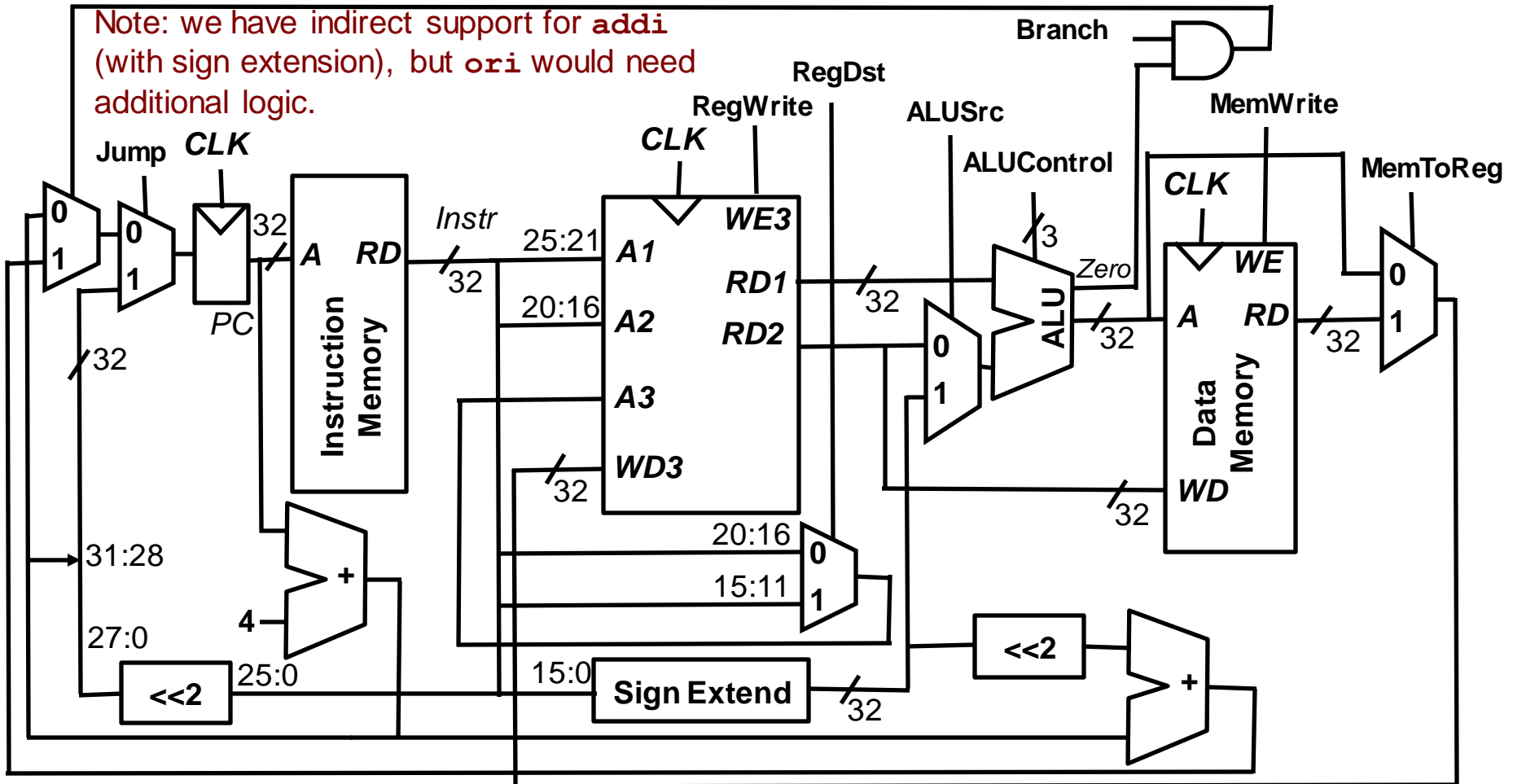

Part III

Control Unit in a Single-Cycle Processor



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.

Part I
Arithmetic
Logic Unit


Part II
Data Path in a
Single-Cycle Processor



Part III
Control Unit in a
Single-Cycle Processor


What to Control?

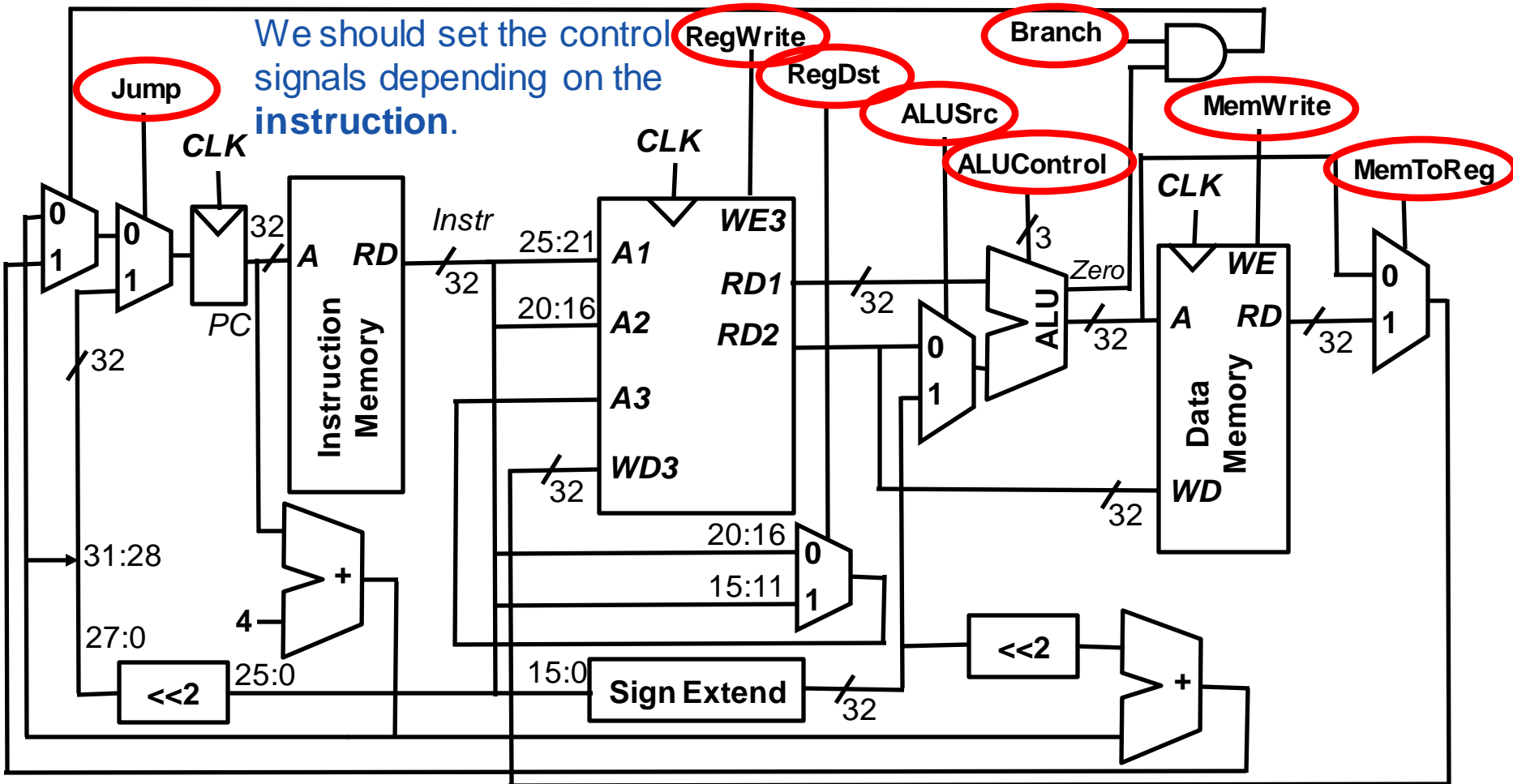We should set the control signals depending on the instruction.




Control Unit Input: Machine Code

R-Type

 


For most R-Type instructions, the op field is 0. The control signals depend on the **funct** field.

I-Type

 

For I-Type and J-Type, the control signals depend on the **op** field

J-Type

 

Control Unit Structure

The 6 bits **op** field from all instruction types

Internal signal ALUOp


ALUOp = 00 means add

ALUOp = 01 means subtract

ALUOp = 10 look at the **funct** field

ALUOp = 11 n/a

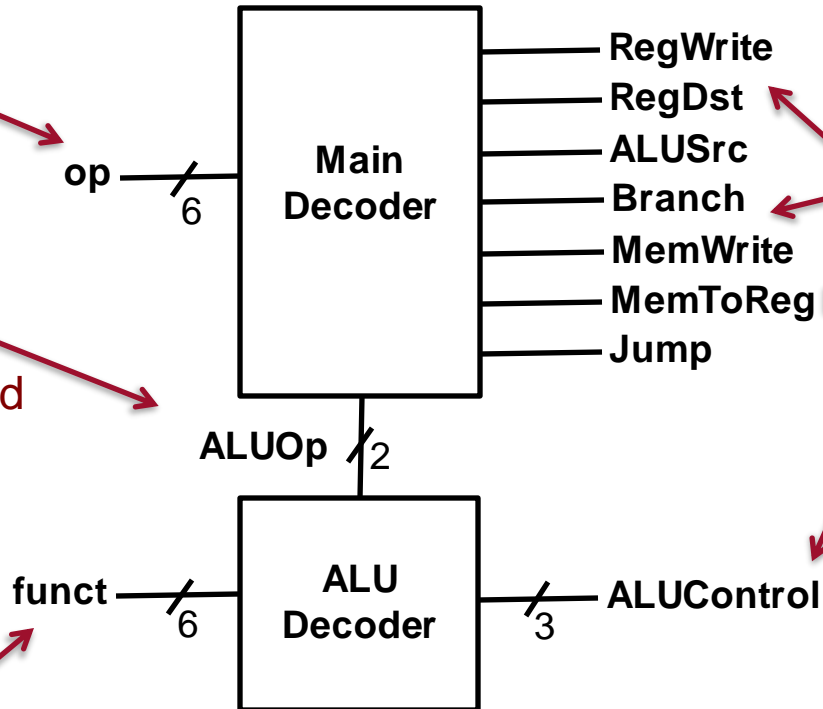
The 6 bits **funct** field from the R-type.
Ignored if other types.



Control signals to the data path

ALU Decoder

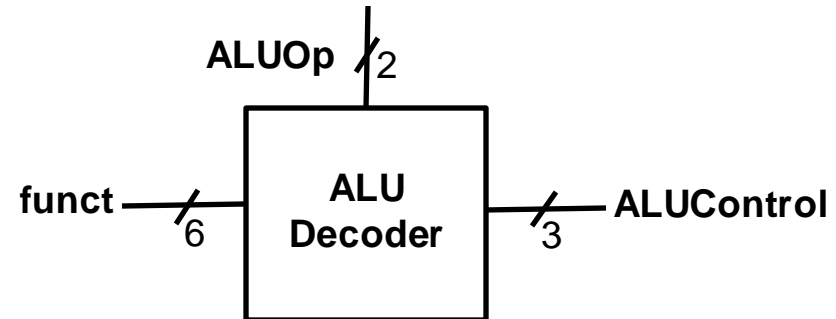Enough to check one bit (faster decoding)



ALUOp	funct	ALUControl
00	?	010 (add)
?1	?	110 (subtract)
1?	100000 (add)	010 (add)
1?	100010 (sub)	110 (subtract)
1?	100100 (and)	000 (and)
1?	100101 (or)	001 (or)
1?	101010 (slt)	111 (set less than)

Main Decoder

Instr	op	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemToReg	Jump	ALUOp
R-Type	000000	1	1	0	0	0	0	0	10
lw	100011	1	0	1	0	0	1	0	00
sw	101011	0	?	1	0	1	?	0	00
beq	000100	0	?	0	1	0	?	0	01
addi	001000	1	0	1	0	0	0	0	00
j	000010	0	?	?	?	0	?	1	??

Performance Analysis (2/2)

Single-Cycle Processor

$$\text{Execution time (in seconds)} = \# \text{ instructions} \times \frac{\text{clock cycles}}{\text{instruction}} \times \frac{\text{seconds}}{\text{clock cycle}}$$

Number of instructions in a program (# = number of)

Determined by programmer or the compiler or both.

Average **cycles per instruction (CPI)**

Determined by the micro-architecture implementation.

Each instruction takes one clock cycle. That is, $\text{CPI} = 1$.


Seconds per cycle = **clock period T_c** .

Determined by the critical path in the logic.

The main problem with this design is the **long critical path**.

The **lw** instruction has longer path than R-Type instructions. However, because of synchronous logic, the clock period is determined by the slowest instruction.

Critical Path Example: Load Word (lw) Instruction

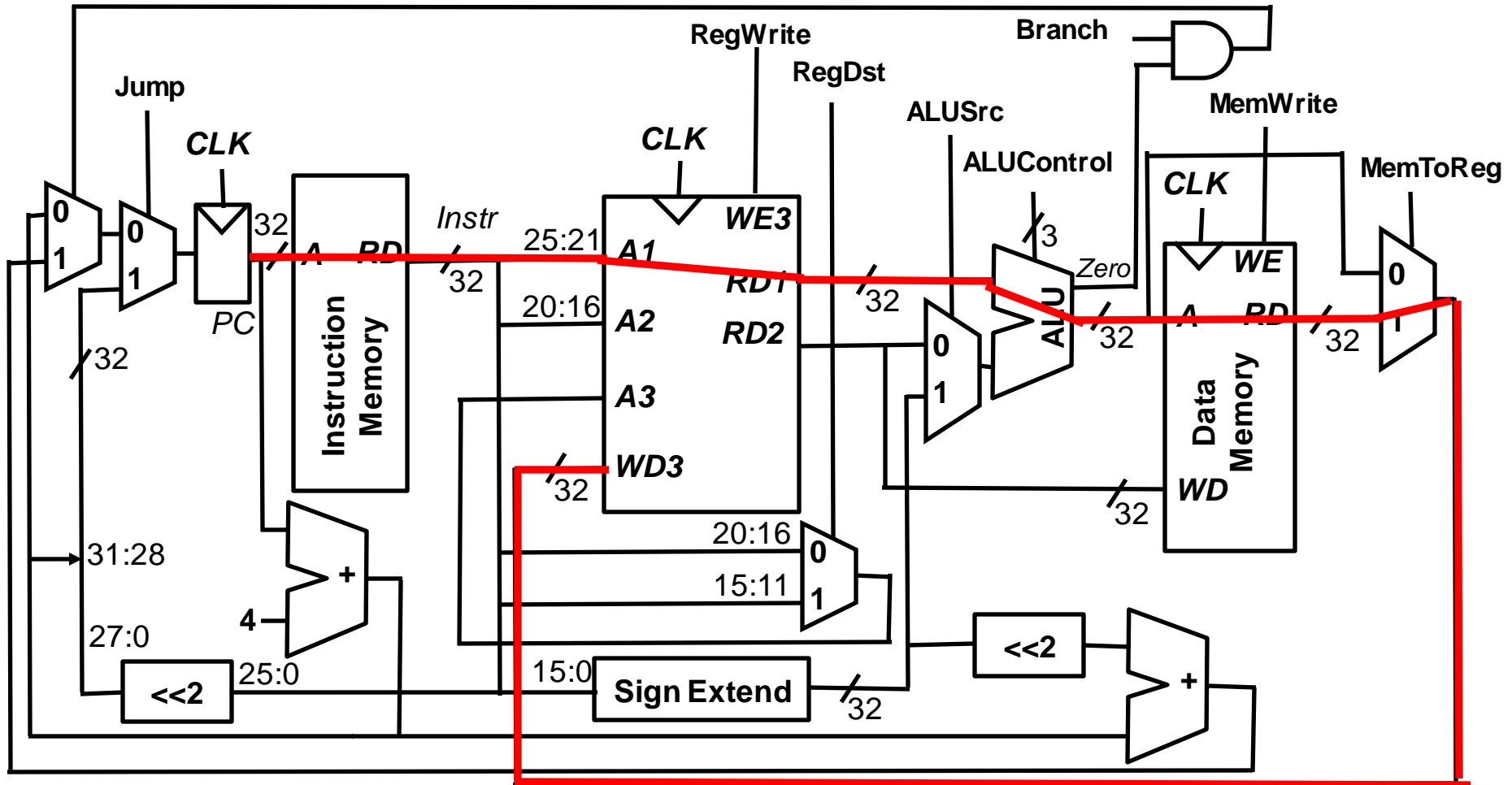

Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor



Part III
Control Unit in a
Single-Cycle Processor



Reading Guidelines



Module 4: Processor Design

Lecture 9: ALU and Single-Cycled Processors

- H&H Chapters 5.2.4, 7.1-7.3.

Lecture 10: Pipelined processors

- H&H Chapters 7.5, 7.8.1-7.8.2, 7.9

Reading Guidelines

See the course webpage
for more information.

Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor



Summary

Some key take away points:

- The **ALU** performs most of the arithmetic and logic computations in the processor.
- The **data path** consists of sequential logic that performs processing of words in the processor.
- The **control unit** decodes instructions and tells the data path what to do.
- The single-cycle processor has a **long critical path**. We will solve this in the next lecture by introducing a **pipelined processor**.



Thanks for listening!

Part I
Arithmetic
Logic Unit

Part II
Data Path in a
Single-Cycle Processor

Part III
Control Unit in a
Single-Cycle Processor