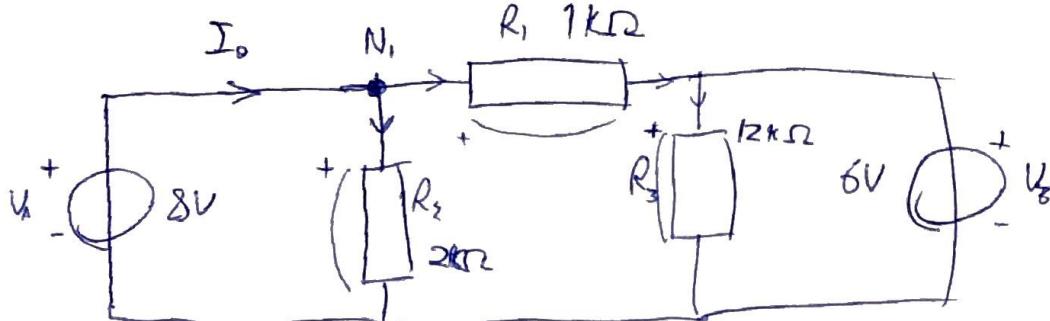


1.



$$KCL: I_o = \frac{U_{o2}}{R_2} + \frac{U_{o1}}{R_1} \quad I_o = \frac{U_{o2}}{2000} + \frac{U_{o1}}{1000}$$


$$KVL: -U_2 + U_1 = 0 \quad U_2 - U_3 - U_1 = 0 \quad U_8 - U_3 = 0$$

$$-U_2 + 8 = 0 \quad 8 = U_3 + U_1 \quad U_3 = 6$$

$$U_1 = 8 - U_3 \quad U_1 = 2$$

$$I_o = \frac{U_2}{R_2} + \frac{U_1}{R_1} = \frac{8V}{2k\Omega} + \frac{2V}{1k\Omega} = 4mA + 2mA = \boxed{6mA}$$

2.

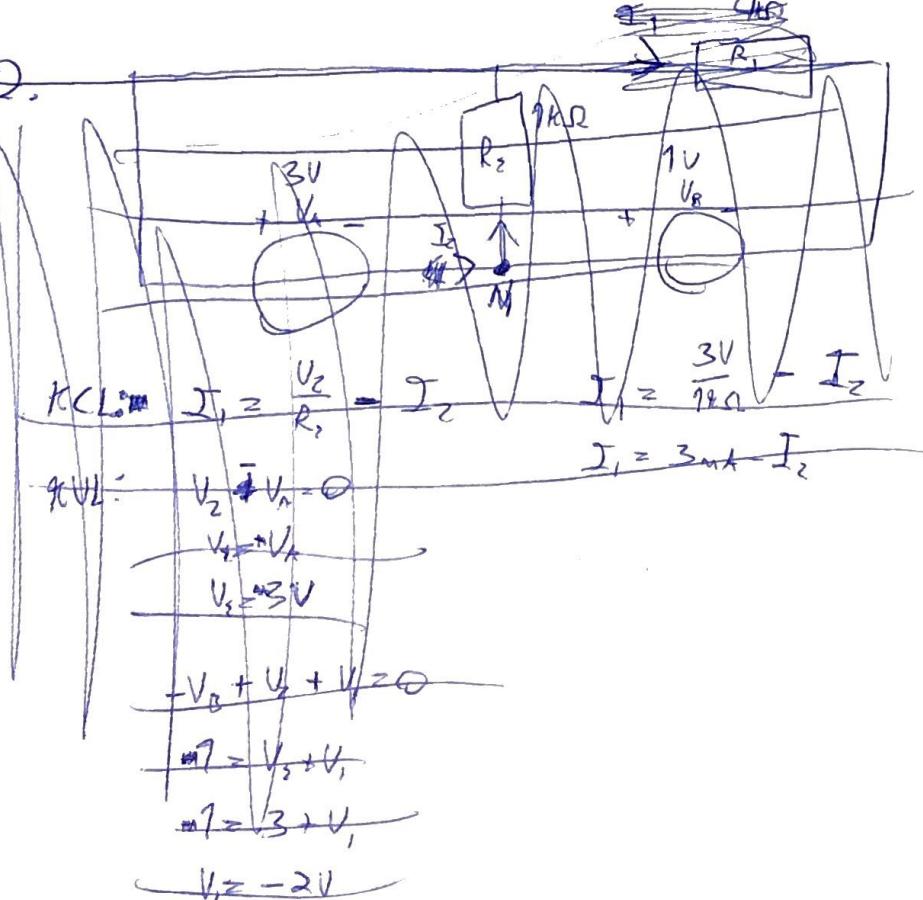

~~$$KCL: I_1 = \frac{U_2}{R_2} = I_2 \quad I_1 = \frac{3V}{9k\Omega} - I_2$$~~

~~$$KVL: V_2 - V_1 = 0 \quad I_1 = 3mA - I_2$$~~

~~$$V_2 = V_1$$~~

~~$$V_1 = 3V$$~~


~~$$-V_0 + U_2 + V_1 = 0$$~~

~~$$-V_0 = V_2 + V_1$$~~

~~$$-V_0 = 3 + V_1$$~~

~~$$V_2 = -2V$$~~

2.

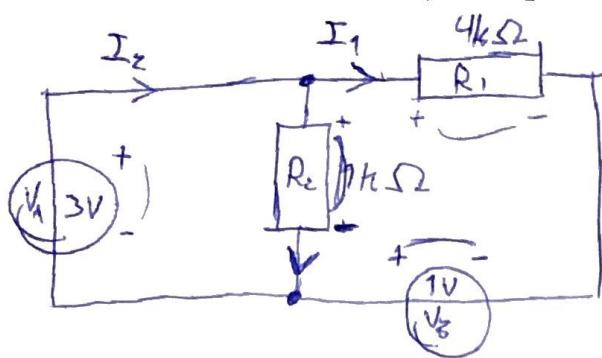

$$\begin{aligned}
 R_1 &= 4\text{k}\Omega \\
 R_2 &= 1\text{k}\Omega \\
 V_A &= 3\text{V} \\
 V_B &= 1\text{V} \\
 I_1 &=? \\
 I_2 &??
 \end{aligned}$$

$$\text{KCL: } -I_1 = -I_2 + \frac{V_2}{R_2}$$

$$I_1 = \frac{V_1}{R_1} = \frac{V_1}{4\text{k}\Omega}$$

$$\Rightarrow -\frac{V_1}{4\text{k}\Omega} = -I_2 + \frac{V_2}{1\text{k}\Omega}$$

$$I_2 = \frac{V_2}{1\text{k}\Omega} + \frac{V_1}{4\text{k}\Omega}$$

$$\text{KVL: } \cancel{V_1 - V_2 = V_B}$$

$$V_2 - V_A = 0$$

$$V_B + V_2 - V_1 = 0$$

$$V_2 = V_A$$

$$V_1 = V_2 + 1$$

$$V_2 = 3\text{V}$$

$$I_2 = \frac{V_2}{1\text{k}\Omega} + \frac{V_2 + 1}{4\text{k}\Omega}$$

$$I_2 = \frac{3\text{V}}{1\text{k}\Omega} + \frac{3+1}{4\text{k}\Omega}$$

$$= 3\text{mA} + 1\text{mA}$$


$$= 4\text{mA}$$

$$I_1 = I_2 - \frac{V_2}{R_2}$$

$$I_1 = 4\text{mA} - 3\text{mA}$$

$$\boxed{I_1 = 1\text{mA}}$$

3.

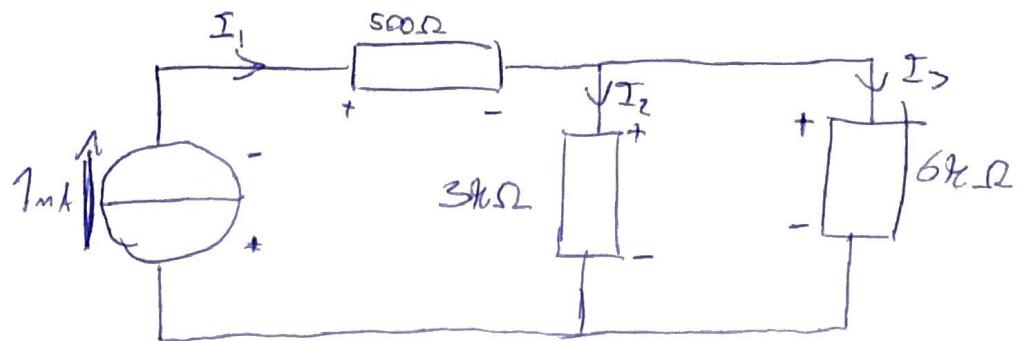

$I_1 = 1 \text{ mA}$ (circuit is in series/conservation of current)

$$\text{KCL: } I_2 + I_3 = I_1 \quad V_2 = 3I_2 \text{ V}$$

$$1 \text{ mA} = I_2 + I_3 \quad V_3 = 6I_3 \text{ V}$$

$$\text{KVL: } V_2 - V_3 = 0$$

$$V_2 = V_3$$

$$3I_2 = 6I_3$$


$$I_2 = 2I_3 \quad \left. \begin{array}{l} I - I_3 = 2I_3 \\ I = 3I_3 \end{array} \right\}$$

$$I_2 = 1 \text{ mA} - I_3$$

$$I_3 = \frac{1}{3} \text{ mA}$$

$$I_2 = 3I_3 = \frac{2}{3} \text{ mA}$$

$$I_1 = 1 \text{ mA}$$

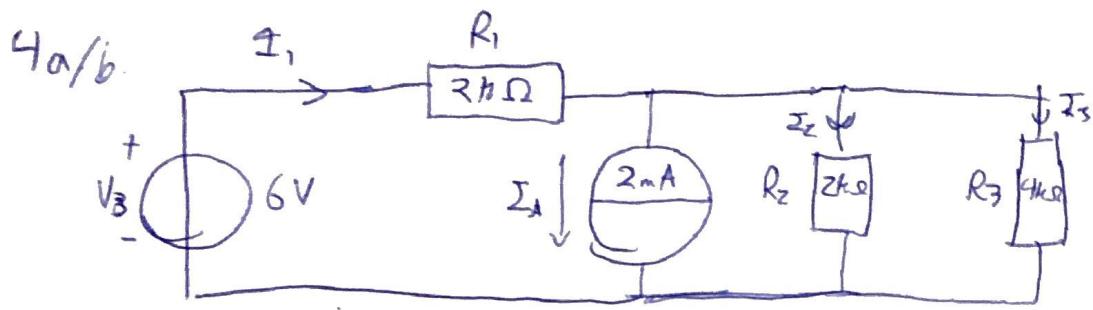

$$V_1 = I_1 R_1 = I_1 \cdot 2k\Omega = 2I_1 \text{ V}$$

$$V_2 = I_2 R_2 = 2mA \cdot 2k\Omega = 2I_2 \text{ V}$$

$$V_3 = I_3 R_3 = I_3 \cdot 4k\Omega = 4I_3 \text{ V}$$

KCL: $I_1 = I_A + I_2 + I_3$

$$I_1 = 2mA + I_2 + I_3$$

KVL: $V_3 - V_2 = 0$

$$4I_3 - 2I_2 = 0$$

$$4I_3 = 2I_2$$

$$I_2 = 2I_3$$

$$I_1 = 2mA + 2I_3 + I_3$$

$$I_1 = 2mA + 3I_3$$

KVL: $V_B = V_1 + V_A = V_1 + V_2 = V_1 + V_3$

$$V_A = V_2 = V_3 = -V_B - V_1$$

$$V_A = 2I_2 = 4I_3 = 6 - 2I_1$$

$$4I_3 = 6 - 2I_1$$

$$2I_1 = 6 - 4I_3$$

$$I_1 = 3 - 2I_3$$

$$3 - 2I_3 = 2 + 3I_3$$

$$1 = 5I_3$$

$$I_3 = \frac{1}{5}mA$$

$$I_2 = \frac{2}{5}mA \quad (2I_3 = \frac{2}{5}mA)$$

$$I_1 = \frac{13}{5}mA \quad (2 + \frac{3}{5} = 2 + 3I_3)$$

$$V_3 = \frac{4}{5}V$$

$$V_2 = \frac{4}{5}V$$

$$V_1 = \frac{26}{5}V$$

	(V)	(mA)	(mW)
	V	I	P
R ₁	5.2	2.6	13.52
R ₂	0.8	0.4	0.32
R ₃	0.8	0.2	0.16
I _A	0.8	2	1.6
V _B	-6	2.6	-15.6

$$I_A = 2mA$$

* V_B = -6V (opposite to current flow)

$$V_A = V_2 = \frac{4}{5}V$$

$$I_B = I_1 \text{ (in series)}$$

$$I_B = \frac{13}{5}mA$$

$$P = IV$$

$$P_1 = 5.2 \cdot 2.6 = 13.52$$


$$P_2 = 0.8 \cdot 0.4 = 0.32$$

$$P_3 = 0.8 \cdot 0.2 = 0.16$$

$$P_A = 0.8 \cdot 2 = 1.6$$

$$P_B = -6 \cdot 2.6 = -15.6$$

5.

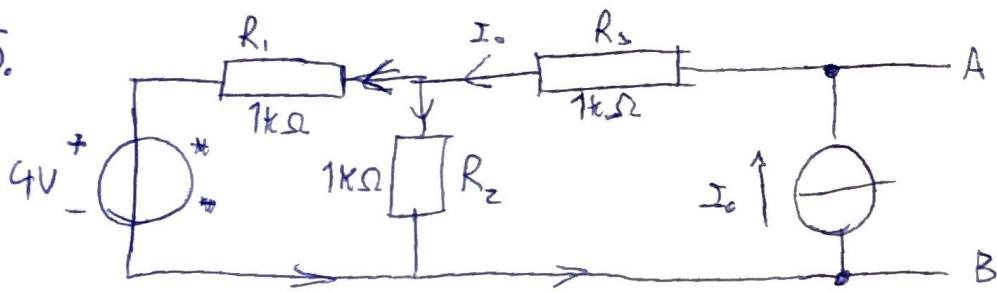

$$\text{d. } I_o = 1 \text{ mA}$$

$$\text{KCL: } I_o = \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_1}{1\text{k}\Omega} + \frac{V_2}{1\text{k}\Omega} = \frac{V_1 + V_2}{1\text{k}\Omega} \quad 1 \text{ mA} = \frac{V_1 + V_2}{1\text{k}\Omega}$$

$$I_o = \frac{V_1 + V_2}{1\text{k}\Omega} \quad 1 \text{ mA} = \frac{V_3}{1\text{k}\Omega} \quad V_3 = 1 \text{ V} \quad V_1 + V_2 = 1 \text{ V} \\ V_2 = 1 - V_1$$

$$\text{KVL: } 4 \text{ V} + V_1 - V_2 = 0$$

$$V_2 = 4 + V_1$$

$$1 - V_1 = 4 + V_1$$

$$2V_1 = -3$$

$$\boxed{\begin{array}{l} V_1 = -1.5 \text{ V} \\ V_2 = 2.5 \text{ V} \\ V_3 = 1 \text{ V} \end{array}}$$

$$\text{KVL: } V_{AB} - V_2 - V_3 = 0$$

$$\boxed{V_{AB} = V_2 + V_3 = 2.5 + 1 \text{ V} = 3.5 \text{ V}}$$

$$\boxed{\begin{array}{l} P_{Q1} = V_1 I_1 = -1.5 \cdot \frac{-1.5}{1\text{k}\Omega} = 2.25 \text{ mW} \\ P_Q = V_{AB} I_o = 3.5 \cdot 1 \text{ mA} = 3.5 \text{ mW} \end{array}}$$

$$\text{b. } I_o = 10 \text{ mA} = \frac{V_1 + V_2}{1\text{k}\Omega} \quad V_1 + V_2 = 10 \text{ V}$$

$$10 \text{ mA} = \frac{V_3}{1\text{k}\Omega} \quad V_3 = 10 \text{ V}$$

$$V_2 = 4 + V_1$$

$$10 - V_1 = 4 + V_1$$

$$2V_1 = 6$$

$$V_1 = 3 \text{ V}$$

$$V_2 = 10 - 3 = 7 \text{ V}$$


$$V_3 = 10 \text{ V}$$

$$V_{AB} - V_2 - V_3 = 0$$

$$\boxed{V_{AB} = V_2 + V_3 = 10 \text{ V} + 7 \text{ V} = 17 \text{ V}}$$

$$\boxed{\begin{array}{l} P_{Q1} = V_1 I_1 = 3 \text{ V} \cdot \frac{3 \text{ V}}{1\text{k}\Omega} = 9 \text{ mW} \\ P_Q = V_{AB} I_o = 17 \text{ V} \cdot 10 \text{ mA} = 170 \text{ mW} \end{array}}$$

6.

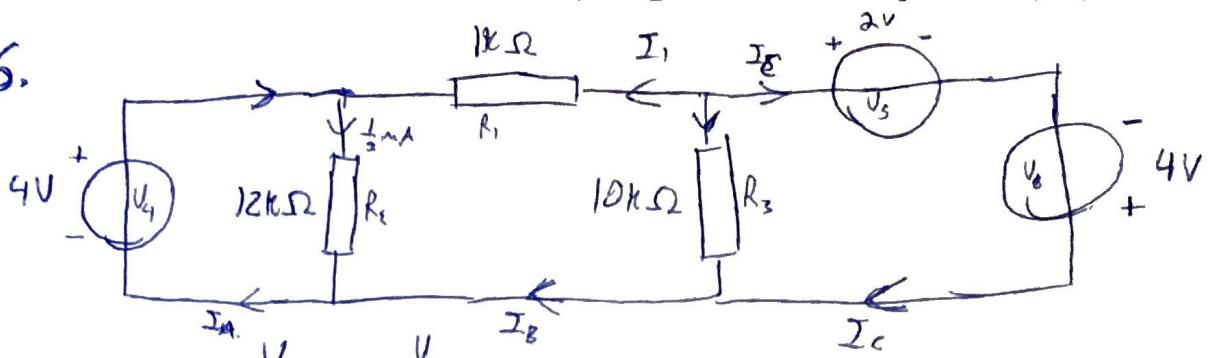

$$I_1 = \frac{V_1}{R_1} = \frac{4V}{1k\Omega}$$

$$-I_1 = I_E + \frac{V_3}{R_3} = I_E + \frac{V_3}{10k\Omega}$$

$$V_5 - V_6 - V_3 = 0$$

$$2 - 4 = V_3$$

$$V_3 = -2V$$

$$-I_1 = I_E - \frac{2}{10k\Omega} = I_E - 0.2mA$$

$$I_1 = 0.2mA - I_E$$

$$\text{KVL: } 4V - V_2 = 0$$

$$V_2 = 4V \quad I_2 = \frac{V_2}{R_2} = \frac{4V}{12k\Omega} = \frac{1}{3}mA$$

~~$I_A = I_1 + I_E$~~

~~$I_B = I_E + I_A$~~

~~$I_B = \frac{1}{3}mA + \frac{1}{3}mA = I_1$~~

~~$I_B = I_1$~~

$$\text{KUL: } V_2 - V_3 + V_1 = 0$$

$$V_1 = V_3 - V_2$$

$$V_1 = -2 - 4 = -6V$$

$$I_1 = \frac{V_1}{R_1} = \frac{-6V}{1k\Omega} = -6mA$$