



# Computer Hardware Engineering (IS1200)

## Computer Organization and Components (IS1500)

Fall 2020


### Lecture 8: Sequential Logic

*Note: This lecture is optional for IS1200 (for review only)*

Artur Podobas

Researcher, KTH Royal Institute of Technology

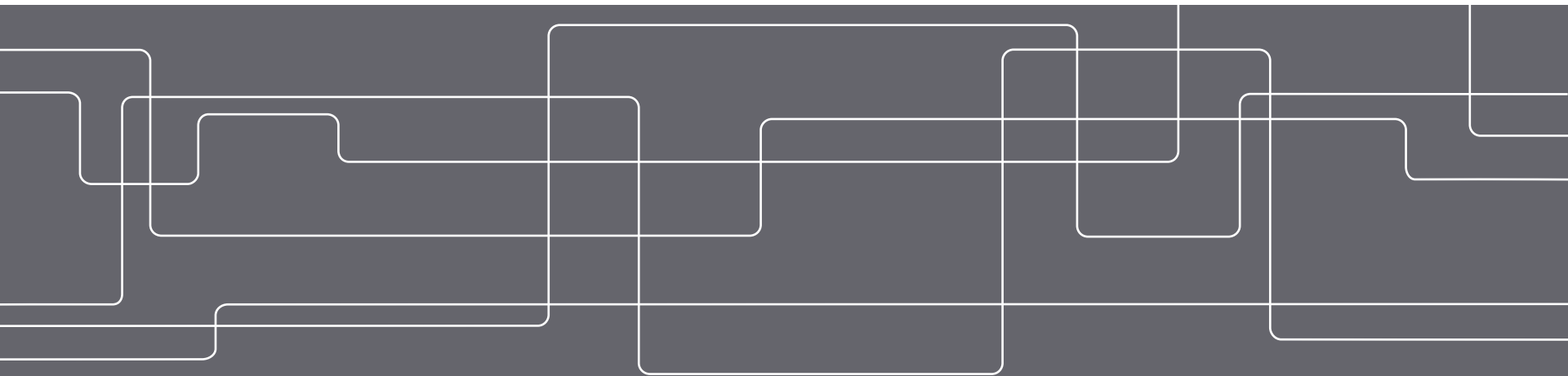Slides by David Broman (extensions by Artur Podobas), KTH






# Course Structure



## Module 1: C and Assembly Programming

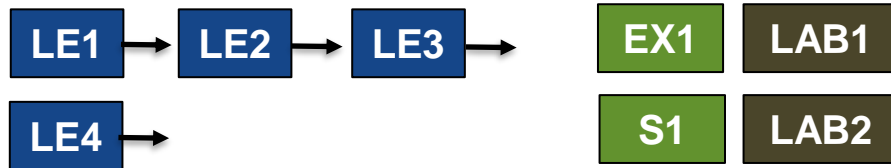


## Module 2: I/O Systems



## Module 3: Logic Design (IS1500 only)




**PROJ  
START**

 

## Module 4: Processor Design



## Module 5: Memory Hierarchy

 

## Module 6: Parallel Processors and Programs



**Proj. Expo**

**LE14**

**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines

# Agenda

## Part I

### Bistability and Latches



## Part II

### Flip-Flops, Registers, and Register Files



## Part III

### Synchronous Sequential Circuits and Finite State Machines



**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines

# Part I

## Bistability and Latches



<http://www.publicdomainpictures.net/view-image.php?image=8284&picture=staplade-stenar&large=1>

Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.



**Part I**  
Bistability and  
Latches

**Part II**

Flip-Flops, Registers,  
and Register Files

**Part III**

Synchronous Sequential Circuits  
and Finite State Machines




# Combinational vs. Sequential Logic



Circuit *without* memory
   
## Combinational Logic Design (previous lecture)

- Output depends *only* on the input.
- There is *no* memory.



Circuit *with* memory

## Sequential Logic Design (this lecture)

- Depends on *both* current and prior input values.
- As a consequence, sequential logic *has* memory.
- Today, we will learn about:

Latches

Flip-Flops

Registers

We will discuss other kinds of memories in course module 5: *Memory hierarchy*.



Part I

Bistability and  
Latches


Part II

Flip-Flops, Registers,  
and Register Files

Part III


Synchronous Sequential Circuits  
and Finite State Machines

 What is the difference between these two circuits?





Answer: None, but both circuits contain a *cycle*.

What is the value of Q?

 

Notation convention: T-connections connect, four way connections do not.

Analysis by considering two cases:

  

Both cases are stable.  
The circuit is **bistable**.


This circuit has 2 stable **states**. Hence, it is a memory that can store **1 bit** of information.

Problem: We cannot decide what to store (there is no input)


 
# SR Latch

What is the behavior of this circuit? Analyze the 4 cases for inputs  $S$  and  $R$ .




$S$  is the SET signal and  $R$  is the RESET signal.

If  $S$  and  $R$  are zero, the circuit “remembers” the previous  $Q$  value, called  $Q_{pre}$ . We have a memory...

$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q_{pre}$	$\bar{Q}_{pre}$
0	1	0	1
1	0	1	0
1	1	0	0

An SR latch can be implemented using different gates. This is the abstract symbol for an SR latch.

 


**Problem 1.** The awkward case  $S=1, R=1$  results in that both  $Q$  and  $\bar{Q}$  are zero.

**Problem 2.** Mixes the issues of *what* and *when* updates are made. It is hard to design large circuits this way.


 
# D Latch


The **D latch** solves the problems with the SR latch. It has one data input  $D$ , and a clock input  $CLK$ .



$CLK$	$D$	$Q$	$\bar{Q}$
0	?	$Q_{pre}$	$\bar{Q}_{pre}$
1	0	0	1
1	1	1	0

The symbol ? means “don’t care”. It is used to simplify truth tables (we can skip one row in this case). Sometimes a symbol **X** or **D** is used to describe “don’t care”.

Symbol describing a D latch:

 

Also called a **transparent latch** or **level-sensitive latch**.

- $CLK = 1$ , the latch is *transparent* ( $D$  flows through to  $Q$ ).
- $CLK = 0$ , the latch is *opaque* (the latch blocks data from flowing through).



**Part I**  
Bistability and Latches

**Part II**


Flip-Flops, Registers, and Register Files

**Part III**

Synchronous Sequential Circuits and Finite State Machines



# Poll: D Latch

 

**POLL:** Which alternative (a)-(d) is the correct behaviour for a D Latch?

**Answer: D**

$CLK$	$D$	$Q$	$\overline{Q}$
0	?	$Q_{pre}$	$\overline{Q}_{pre}$
1	0	0	1
1	1	1	0



**Part I**  
Bistability and Latches

**Part II**  
Flip-Flops, Registers, and Register Files

**Part III**  
Synchronous Sequential Circuits and Finite State Machines

# Part II

## Flip-Flops, Registers, and Register Files



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.

**Part I**  
Bistability and  
Latches




**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines

# D Flip-Flop


A flip-flop is **edge-triggered** and not level-triggered.

 

**Case I:** CLK = 0

The master is transparent and the slave is opaque.  $D_{in}$  flows to  $N$ .

These symbols describe D Flip-Flops.

 



The **D flip-flop** (the standard flip-flop) copies D to Q on the **rising edge**, and remembers its state all other times.

**Case II:** CLK = 1

The slave is transparent and the master is opaque.  $N$  flows to  $Q_{out}$ .

  
# Resettable and Enabled Flip-Flops

A **resettable flip-flop** resets the flip-flop to 0 when a reset signal is active.



The line above the signal name shows that the reset signal is **active low**: The reset is active on 0.

 An **enabled flip-flop** has an input *EN*. Its state changes only when  $EN = 1$  and there is a raising clock edge (Called WR in the exercise).



True or False Q/A

“This resettable flip-flop is **synchronously resettable**, meaning that it resets on a rising clock edge. It is is not **asynchronously resettable** where the reset is independent of the clock.”

Answer: True



Part I

Bistability and Latches




Part II

Flip-Flops, Registers, and Register Files

Part III

Synchronous Sequential Circuits and Finite State Machines

# Poll: D Flip-Flop

 

**POLL:** Which alternative (a)-(d) is the correct behaviour for a D Flip-Flop?

**Answer: C**




**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines

# D Latch vs D Flip-Flop

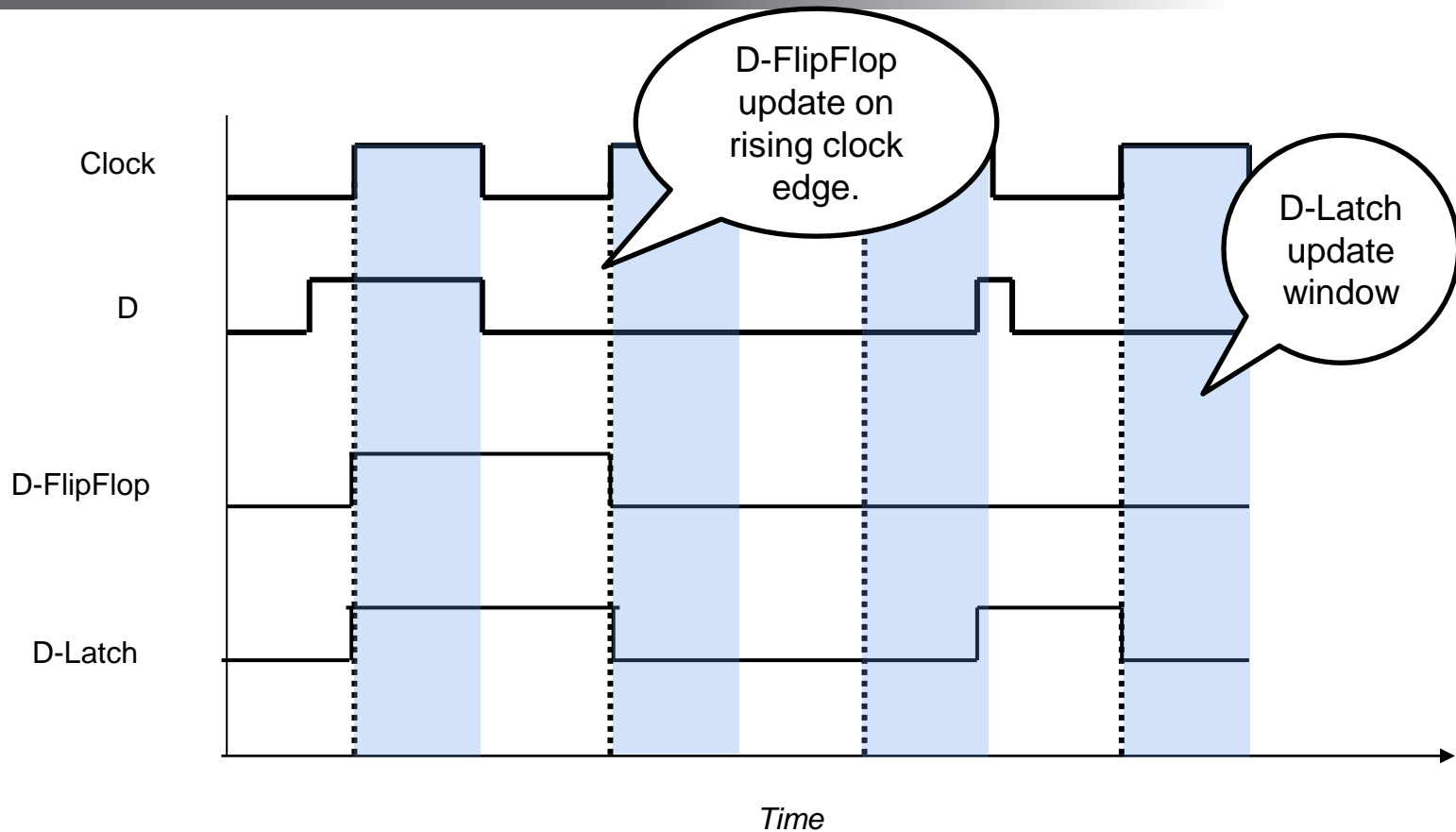


**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files


**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines
 
# Register

An **N-bit register** consists of N flip-flops that share the same clock input.



 4-bit register built out of D flip-flops (using condensed symbol notation).




Abstract form of a 4-bit register.

Note that registers can also have enable signals, reset signals etc.
 
# Output Enable Register


Recall the **tristate** buffer with floating value (Z)



## Exercise:

Create a 2-bit register that has an **output enable (OE)** input signal. If  $OE = 0$  then  $Q$  is floating, else it outputs the registers' state.

## Answer:

 



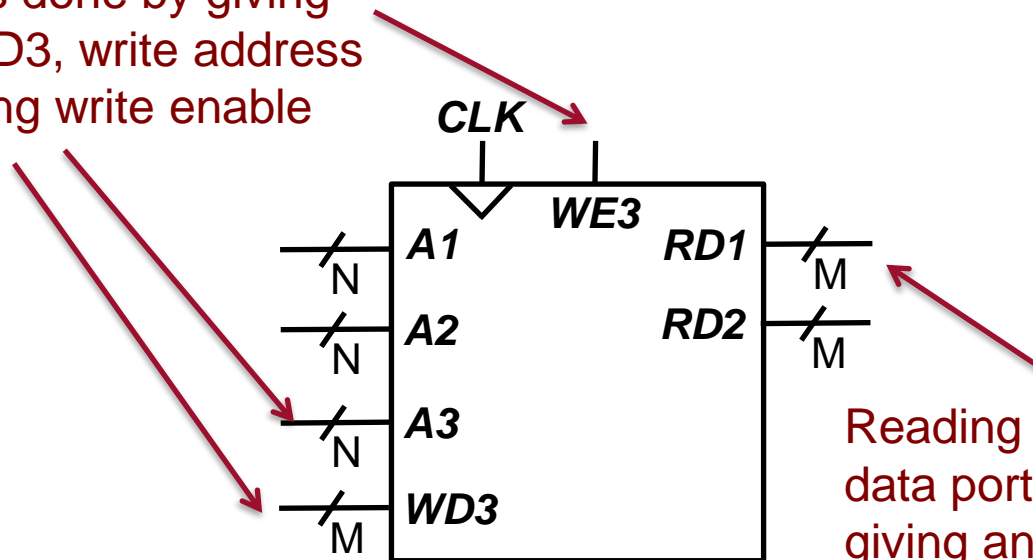
# Register File (1/2)

A **register file** can be used to read and write data using an address.


Writing **M** bits is done by giving write data to WD3, write address to A3, and setting write enable WE3 to 1.



Reading **M** bits from read data port RD1 is done by giving an **N**-bit read address to A1. Same for the second read port (RD2 and A2).


This is a **multi-ported** register file. Two read ports and one write port. Reads and writes can be done in parallel.

# Register File (2/2)

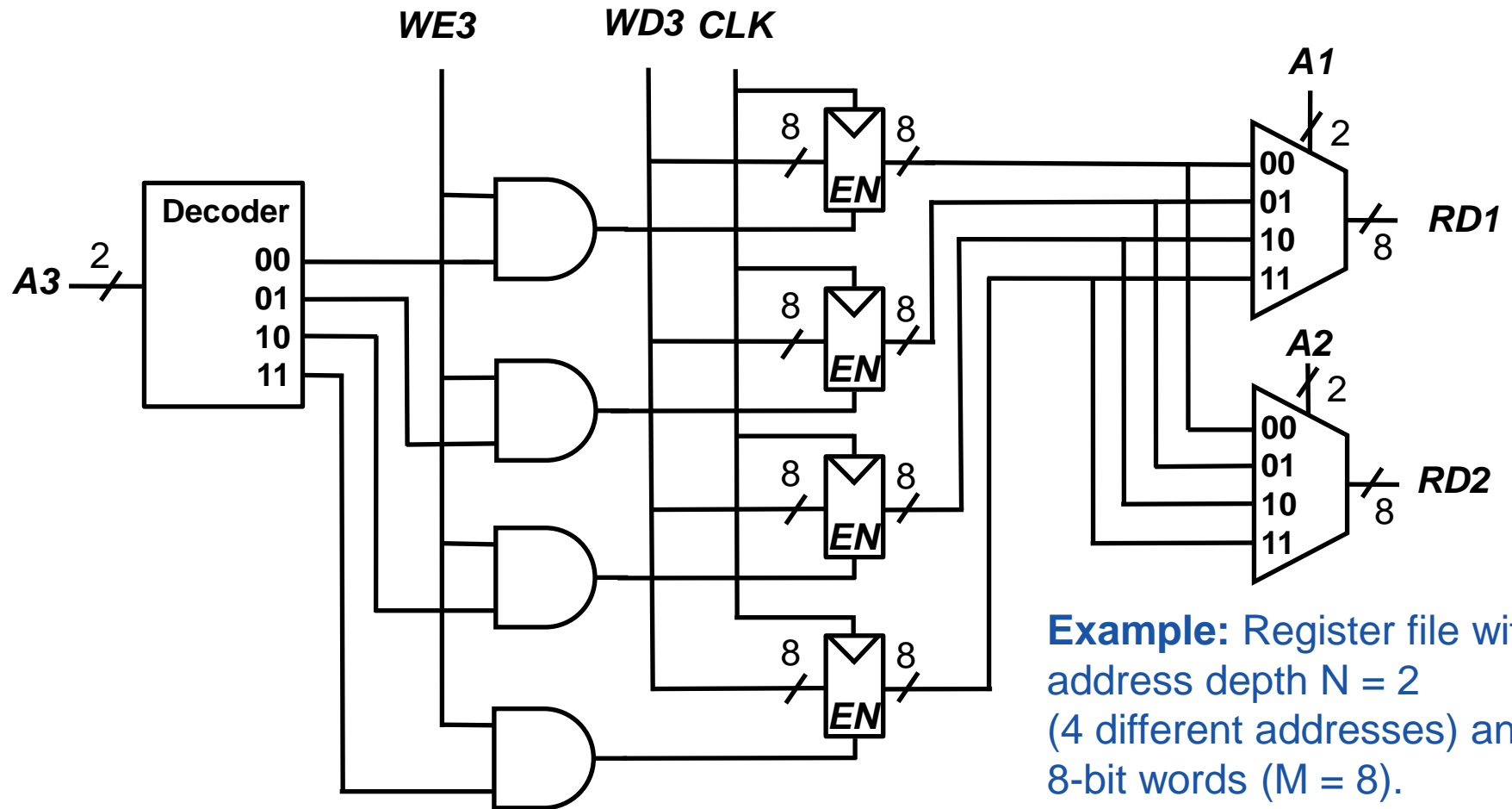

## Part III
 
# Synchronous Sequential Circuits and Finite State Machines



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.

**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files



**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines


# Register-Transfer Level - Synchronous Sequential Circuits

It is hard to analyze large asynchronous circuits that contain cycles.


Solution: Design **synchronous sequential circuits**, also called designing at the **register-transfer level (RTL)**, which means that

- combinational logic is combined with registers
- states are only updated on clock edges

 
Which of the following circuits are using RTL design / sequential synchronous logic?



Yes, with no feedback

 

No, because of latch.

 


No, has a cycle without register in the path

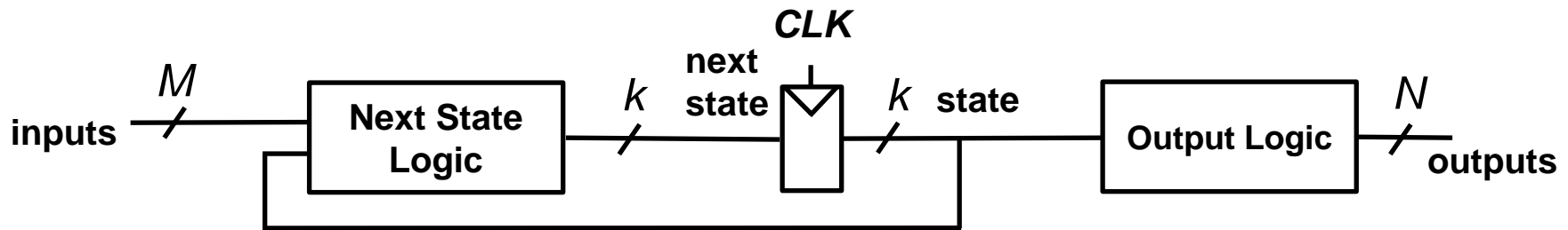
# Finite State Machines (FSMs)

Synchronous Sequential Logics can be defined as FSMs


**Moore Machine** ( $M$  inputs,  $N$  outputs,  $k$  states)



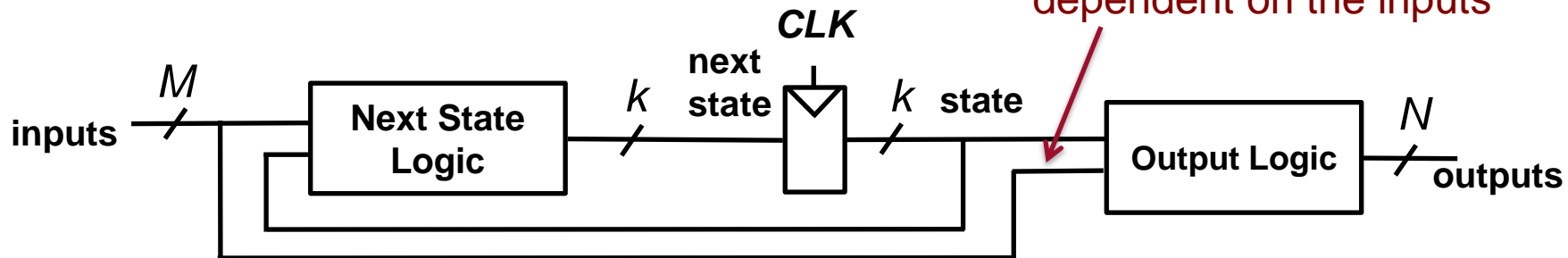**Mealy Machine** ( $M$  inputs,  $N$  outputs,  $k$  states)




# A Simple Mealy Machine Example

 

<i>clock</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>Q</i>	<i>D</i>	<i>Y</i>
init	1	1	0	1	0	1
1 <sup>st</sup>	1	1	1	0	1	1
2 <sup>nd</sup>	1	0	0	1	0	1

After 1<sup>st</sup>, 2<sup>nd</sup> etc.  
positive clock edge.

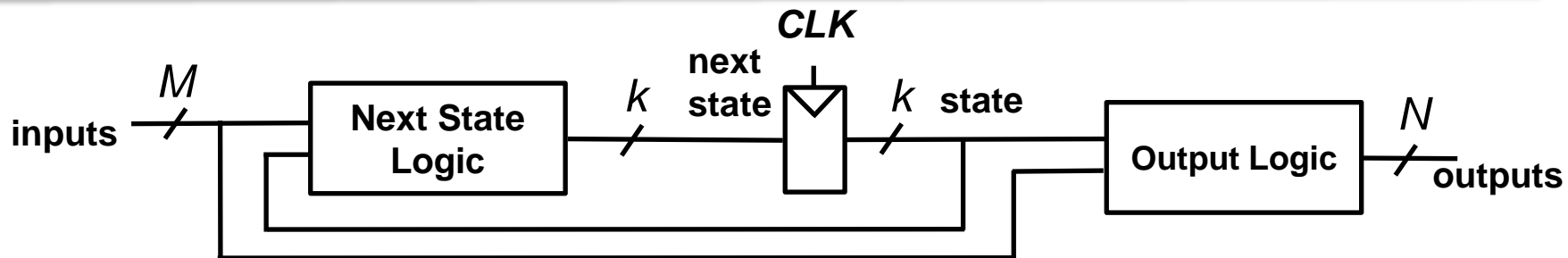

**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files



**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines

# Edge-Triggered Timing Methodology

## How fast can we run a circuit?

The clock period must be longer than the worst-case of delays in the circuit.

A **race** may occur when the values of state elements depend on the relative speed of logic elements in the circuit.

$$\text{delay} = t_{\text{prop}} + t_{\text{combinational}} + t_{\text{setup}} + t_{\text{skew}}$$


Time to propagate through the flip-flop or register.

The longest delay in the combinational logic.

Necessary time before the rising clock edge.

Compensate for **clock skew**: clock signals reach state elements at different time.

The worst-case delay is computed for the feedback loop through the next state logic.

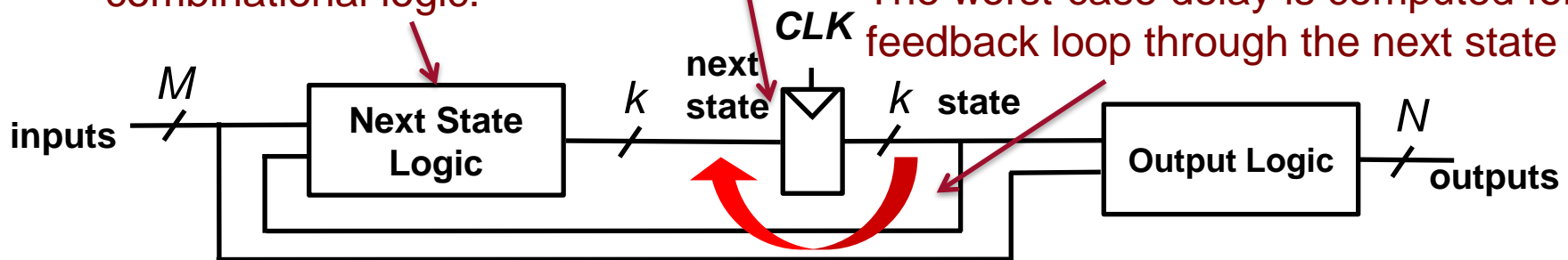

**Part I**  
Bistability and Latches

**Part II**  
Flip-Flops, Registers, and Register Files

**Part III**  
Synchronous Sequential Circuits and Finite State Machines

# We are soon done!



**Part I**  
Bistability and  
Latches


**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines





# Reading Guidelines

 

## Module 3: Logic Design

### Lecture 7: Combinational Logic Design

- H&H Chapters 1.5, 2.1-2.4, 2.6, 2.8-2.9

### Lecture 8: Sequential Logic Design

- H&H Chapters 3.1-3.3 (not 3.2.7), 3.4.1-3.4.3, 5.2.1-5.2.2, 5.5.5

## Reading Guidelines

See the course webpage  
for more information.

**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines

# Summary

## Some key take away points:

- **Combinational Logic vs. Sequential Logic:** Combinational logic has *no* memory, whereas sequential logic *includes* memory.
- **Latches vs. Flip-Flops vs. Registers vs. Register File**  
Flip-flops are edge triggered, registers combine flip-flops, and register files use addresses to access data.
- **Synchronous vs. Asynchronous Logic Design**  
Synchronous Design makes design work easier.
- **Mealy vs. Moore Machines**  
Both are finite state machines (FSMs). Moore machines depend only on the state, whereas Mealy machines depend on the state and the input.



**Thanks for listening!**

**Part I**  
Bistability and  
Latches

**Part II**  
Flip-Flops, Registers,  
and Register Files

**Part III**  
Synchronous Sequential Circuits  
and Finite State Machines